

## LABORATORY WORK SHEET

Name of the Student : Abdul Basith Khan  
 Class : 1<sup>st</sup> Year (CSM-A) Semester : I<sup>st</sup>  
 Course Code : AEE D01 Course Name : EEE Laboratory  
 Name of the Course Faculty : Dr. L. Rajashekhara Goud Faculty ID : IARE11067  
 Exercise Number : 08 Week Number : 08 Date : 17/01/2024

Roll Number									
2	3	9	5	1	A	6	6	0	1

### DAY TO DAY EVALUATION:

Marks	Aim / Preparation	Algorithm / Procedure	Source Code	Program Execution	Viva - Voce	Total
		Performance in the Lab	Calculations and Graphs	Results and Error Analysis		
Max. Marks	4	4	4	4	4	20
Obtained	4	4	4	3	4	19

Signature of Faculty

### START WRITING FROM HERE :


Swinburnes Test :-

Aim:-

Pre-determine the efficiency and constant losses of a DC shunt machine by Swinburnes Method.

Apparatus:-

S. No	Name of the Equipment	Type	Range	Quantity
1.	Ammeter	MC	0-20 A	1
2.	Voltmeter	MC	0-300 V	1
3.	Ammeter	MC	0-2 A	1
4.	Rheostat	Wire wound	370 $\Omega$ / 1.7 $\Omega$	1
5.	Connecting Wires	-	-	-

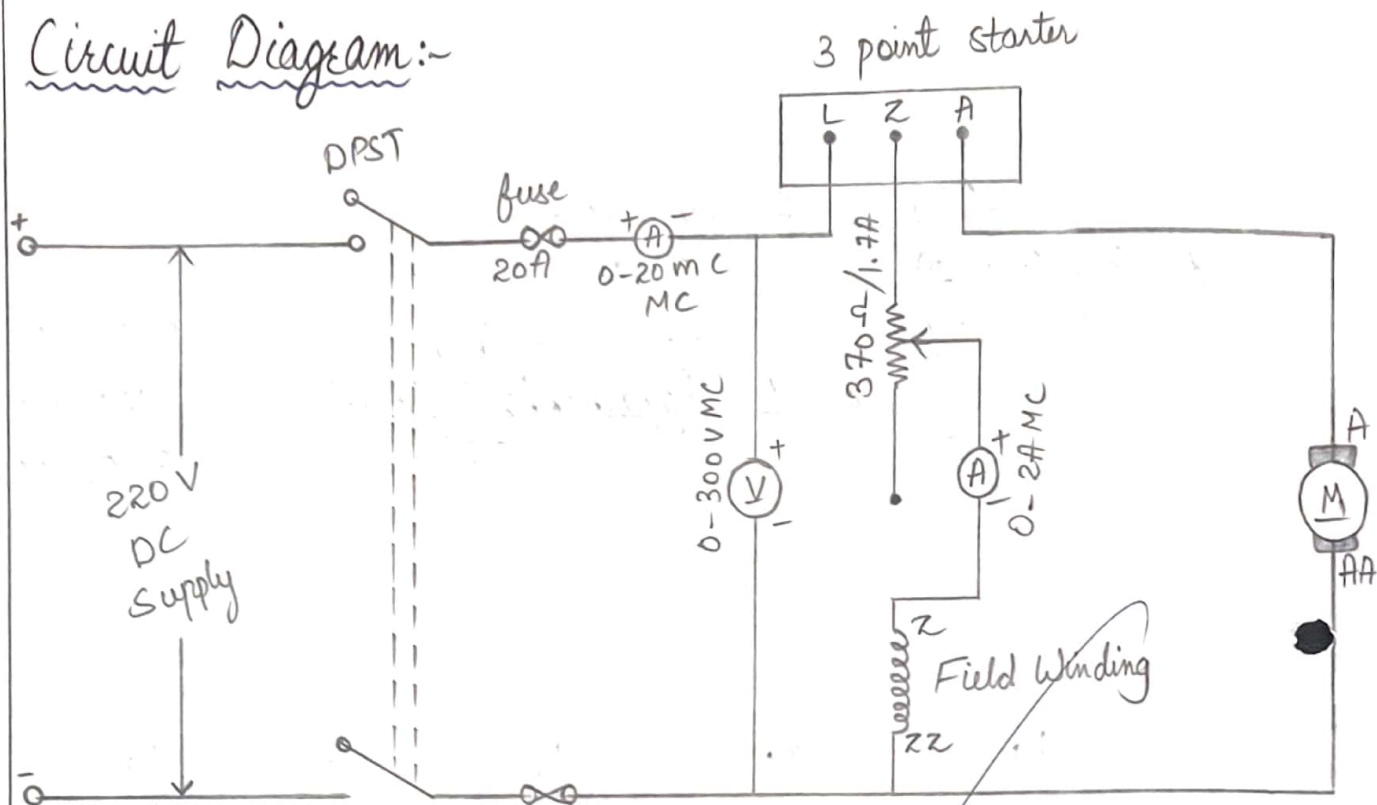Circuit Diagram:-

Swinburn's test on DC Shunt motor.

Name Plate Details:-  
Motor.

Voltage	230 V
Current	19 A
Output	5 HP
Speed	1500 rpm

Procedure:-

1. Choose the proper ranges of meters after noting the name plate details of the given machine and make the connections as per the circuit Diagram.
2. Keep the motor field rheostat ( $R_f$ ) in the minimum start the motor by choosing the switch and operating the starter slowly.

3. Run the motor at rated speed by adjusting the motor field rheostat.

4. Note down the voltages no load current and field current calculation for Swinburnes test:-

from the no load test results

supply voltages =  $V_L$  Volts

No load line current =  $I_L$  Amperes

field current =  $I_f$  Amperes

Therefore No load armature current =  $I_{a0} = I_L - I_f$  Amperes

armature Resistance =  $R_a$  :  $R_a = 1.25 \text{ ohms}$

No load Copper losses are =  $I_{a0}^2 R_a$

No load power input =  $V_L I_L$

Constant losses = (No load power input - No load copper losses)

Tabular Column:-

S. No.	V (Volt)	$I_L$ (Amp)	$I_f$ (A)	Speed (rpm)	$R = 1.25 \Omega$
1	230	1.4	0.7	1500	

As a motor Rated Voltage  $V_L = 230$



Sl No.	Volt S.No. (V)	$I_L$ (A)	$I_f$ (A)	$P_c$ Input Power ( $V_L - I_L$ ) (Watt)	$W_c$ Constant losses ( $W_{const}$ ) Watts	Copper losses $W_{Cu} = I_a^2 R_a$ (W)	Total losses ( $W_{const} + W_{Cu}$ ) (W)	O/P Power = (i/p - Total losses) (W)	$P_o = V I_L - W_c - I_a^2 R_a$ $\frac{P_o}{P_i} \times 100$ n%
1.	234	1.4	0.7	322	321.4	0.61	322	0	0
2.	237	2	0.7	460	321.4	2.11	323.51	136.49	29.67
3.	237	4	0.7	1920	321.4	13.61	335.61	584.39	63.8
4.	237	5	0.7	1150	321.4	23.11	344.51	805.49	70.04
5.	237	7	0.7	1610	321.4	49.61	371.01	1238.5	76.92


As a generator Rated Voltage  $V_L = 237$

Sl No.	Volt S.No. (V)	$I_L$ (A)	$I_f$ (A)	Output Power ( $V_L \cdot I_L$ )	Constant losses $W_{const}$	Copper losses $W_{Cu} = I_a^2 R_a$	Total losses ( $W_{const} + W_{Cu}$ )	Input power (output power + losses)	$\eta$
1.	237	1.4	0.7	322	321.4	5.51	326.91	648.91	49.6
2.	237	2	0.7	460	321.4	9.11	330.51	790.51	58.19
3.	237	4	0.7	920	321.4	27.61	349.01	1269.01	72.49
4.	237	5	0.7	1150	321.4	40.61	362.01	1512.01	76.05
5.	237	7	0.7	1610	321.4	74.11	395.51	2005.51	80.3

Scale

On X-axis unit = 100m

On Y-axis unit = 1cm

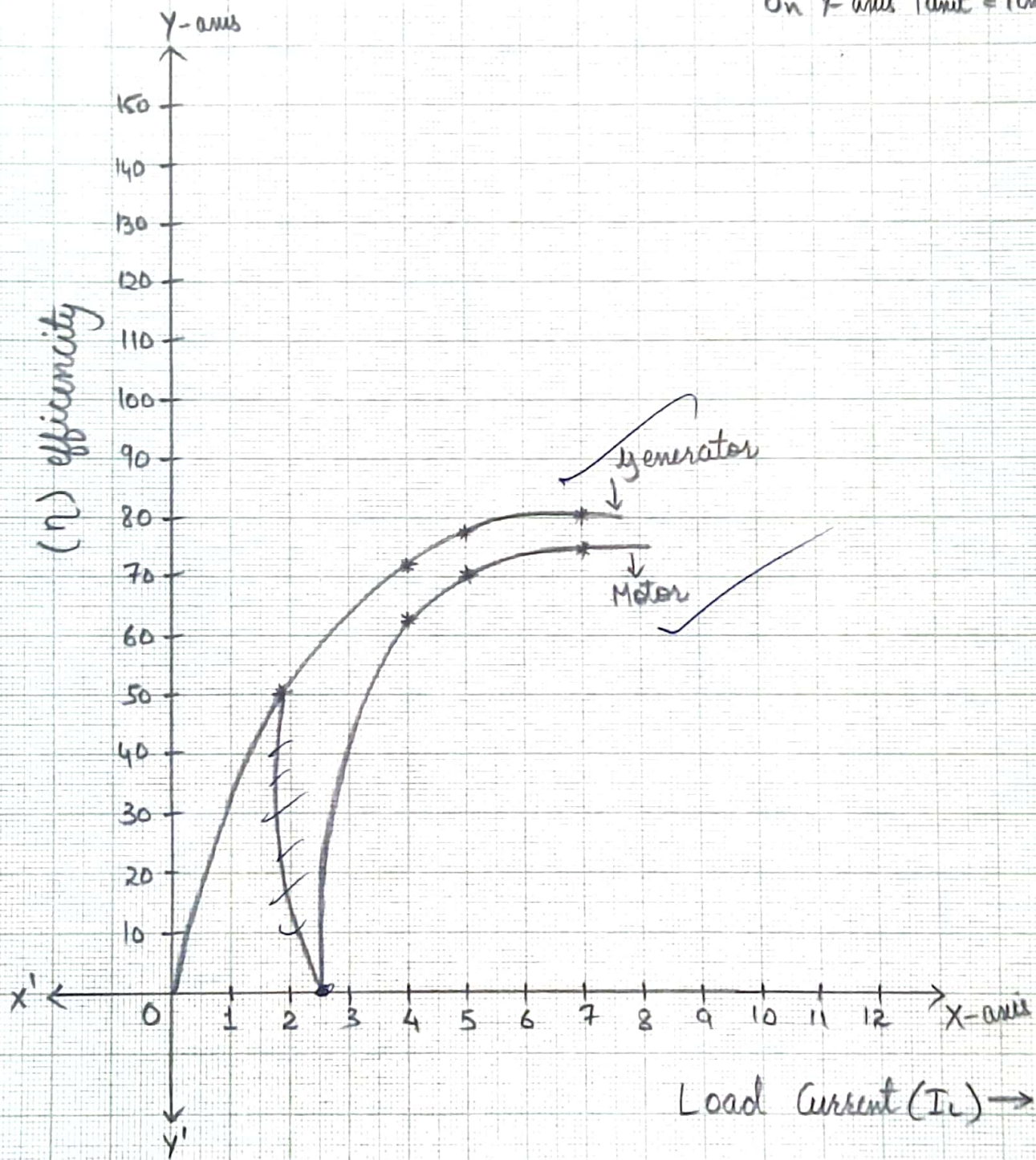



## LABORATORY WORK SHEET

Name of the Student : Abdul Basith Khan  
 Class : 1<sup>st</sup> Year (CSM-A) Semester : I<sup>st</sup>  
 Course Code : AEED01 Course Name : EEE Laboratory  
 Name of the Course Faculty : Dr. L Rajashekhar Goud Faculty ID : IARE/110.67  
 Exercise Number : 08 Week Number : 08 Date : 17/01/2024

Roll Number									
2	3	9	5	1	A	6	6	0	1

### DAY TO DAY EVALUATION:

Marks	Aim / Preparation	Algorithm / Procedure	Source Code	Program Execution	Viva - Voce	Total
		Performance in the Lab	Calculations and Graphs	Results and Error Analysis		
Max. Marks	4	4	4	4	4	20
Obtained						

Signature of Faculty

### START WRITING FROM HERE :

#### Efficiency as Motor:-

Efficiency = output / input = (input - total losses) / input  
 Where total losses = Constant losses + Variable losses

Constant losses are known value from the equation ①

Variable loss =  $I_a^2 R_a$  where  $I_a = I_L - I_f$

Input =  $V_L I_L$   $V_L$  is rated voltage of the machine, Assume line currents ( $I_L$ ) as 2, 4, 6, ..., 20A and find corresponding efficiency.

#### Efficiency as Generator:-

Efficiency = output / input = output / (output + total losses)

where losses = constant losses + variable losses.

Constant losses are same for both motor and generator

Armature current,  $I_a = I_L + I_f$

Variable loss =  $I_a^2 R_a$

Output power =  $V_L I_L$ .  $V_L$  is rated voltage of the machine

Assume load current ( $I_L$ ) as 2, 4, 6, ..., 20A and find corresponding efficiencies.

Calculations:-

$$V_{in} = 230, \quad I_{L0} = 1.4, \quad I_f = 0.7$$

$$\text{Speed} = 1500 \text{ rpm}$$

$$\begin{aligned} \text{No-load Input} &= V_{in} I_{L0} \\ &= 230 \times 1.4 \\ &= 322 \text{ W} \end{aligned}$$

$$I_a = I_L - I_f = 1.4 - 0.7 = 0.7$$

$$R_a = 1.25 \Omega$$

$$\begin{aligned} \text{Variable losses} &= I_a^2 R_a \\ &= (0.7)^2 \times 1.25 \\ &= 0.61 \end{aligned}$$

No load input = Constant losses + Variable losses ( $C_u$ )

$$W_c = V_{in} \cdot I_{L0} - I_a^2 R_a$$

$$W_c = 322 - 0.61$$

$$W_c = 321.4 \text{ W}$$

$$\text{Rated current} = 11 \text{ A}$$

$$\text{Assuming } I_L = 1.4$$

$$V = 230 \quad I_L = 10 \text{ A}$$

$$I_f = (0.7 \text{ A})$$


$$I_a = I_L - I_f = 1.4 - 0.7 = 0.7 \text{ A}$$

$$\text{Total input} = V I_L = 230 \times 1.4 = 322 \text{ A}$$

$$W_c = 321.4 \text{ W}$$

$$\text{Copper losses} = I_a^2 R_a = 0.7^2 \times 1.25 = 0.61$$

$$\begin{aligned} \eta &= \frac{\text{output}}{\text{Input}} = \frac{\text{Input} - \text{losses}}{\text{Input}} = \frac{V I_L - [W_c + I_a^2 R_a]}{V I_L} \\ &= \frac{322 - 322}{322} = 0\% \end{aligned}$$

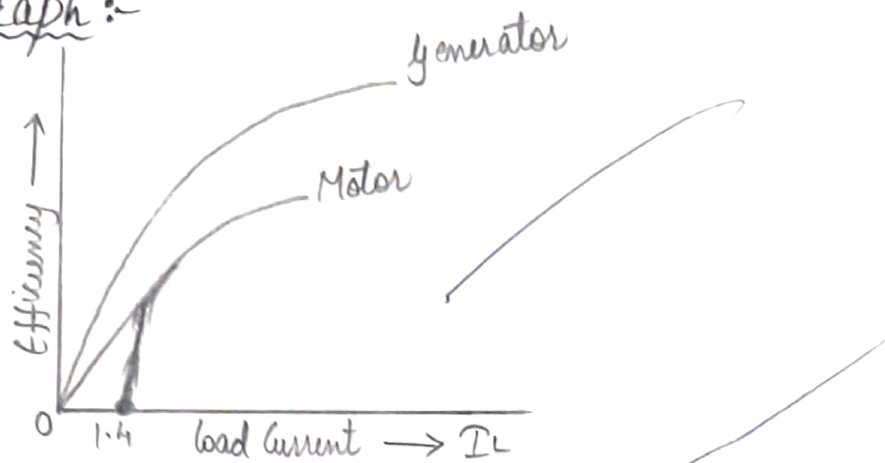Model graph:-Precautions:-

1. Run the motor at rated speed and rated Voltage
2. Avoid loose Connections and Parallel errors.

Result:-

Hence Verified the efficiency and constant losses at DC shunt machine by Swinburn's test.