



LABORATORY WORK SHEET

Name of the Student: MADKI SAI CHARAN

Class: C5M-1C Semester: Ist

Course Code: AEE D03 Course Name: Electrical and Electronics Engineering Laboratory

Name of the Course Faculty: MS. M. VARALAKSHMI Faculty ID: IARE 11072

Exercise Number: 02 Week Number: 02 Date: 3 November 2023

DAY TO DAY EVALUATION:

Marks	Aim / Preparation	Algorithm / Procedure	Source Code	Program Execution	Viva - Voce	Total
		Performance in the Lab	Calculations and Graphs	Results and Error Analysis		
Max. Marks	4	4	4	4	4	20
Obtained	4	4	4	4	4	20

Signature of Faculty


START WRITING FROM HERE: MESH ANALYSIS

Aim : To study of mesh analysis is the objective of this exercise, specifically its usage in multi-source DC circuits. Its applications finding Circuit currents and voltages will be investigated.

Apparatus :


S.NO	EQUIPMENT	RANGE	TYPE	QUANTITY
01.	Resistors	(0-100-2)	-	03.
02.	Ammeter	(0-200mA)	Digital	03.
03.	R.P.S	(0-30V)	Digital	01.
04.	Bread Board	-	-	01.
05.	Connecting wires	-	-	As required

Circuit diagram:

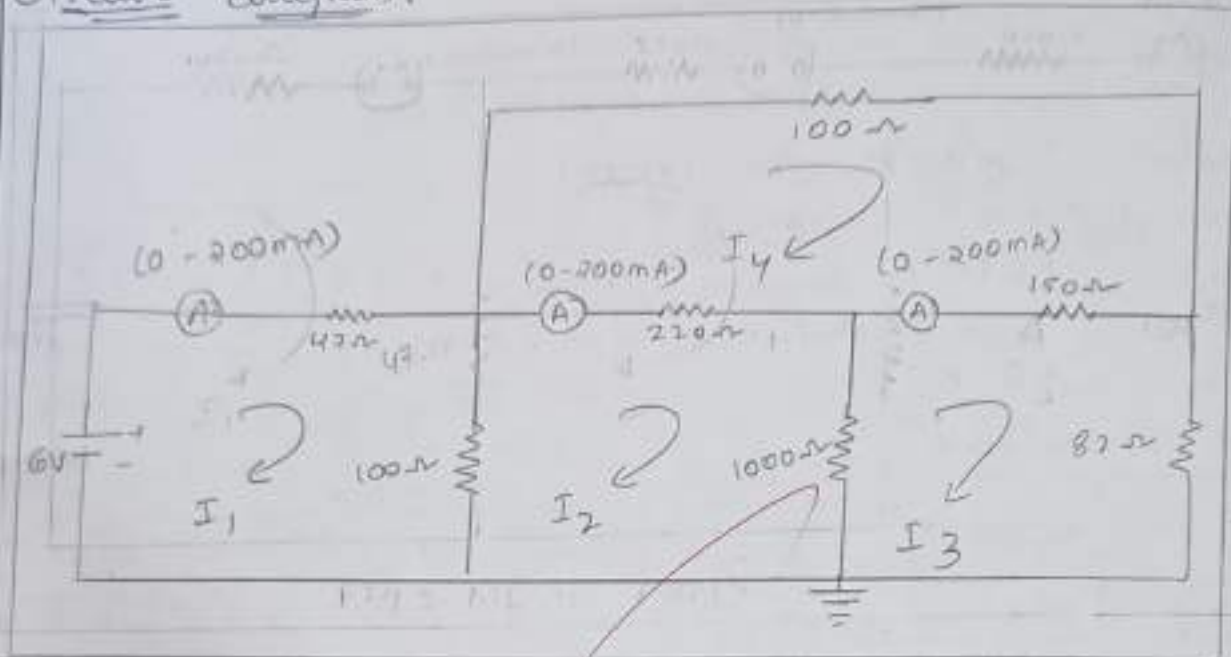

Procedure:

- ① Connect the circuit diagram as show in figure.
- ② Switch on the supply to RPS
- ③ Apply the voltage.
- ④ Gradually increase the supply voltage in steps.
- ⑤ Connect Ammeter in the loop and find the currents I_1, I_2 .
- ⑥ Verify with theoretical result obtained with practical result.

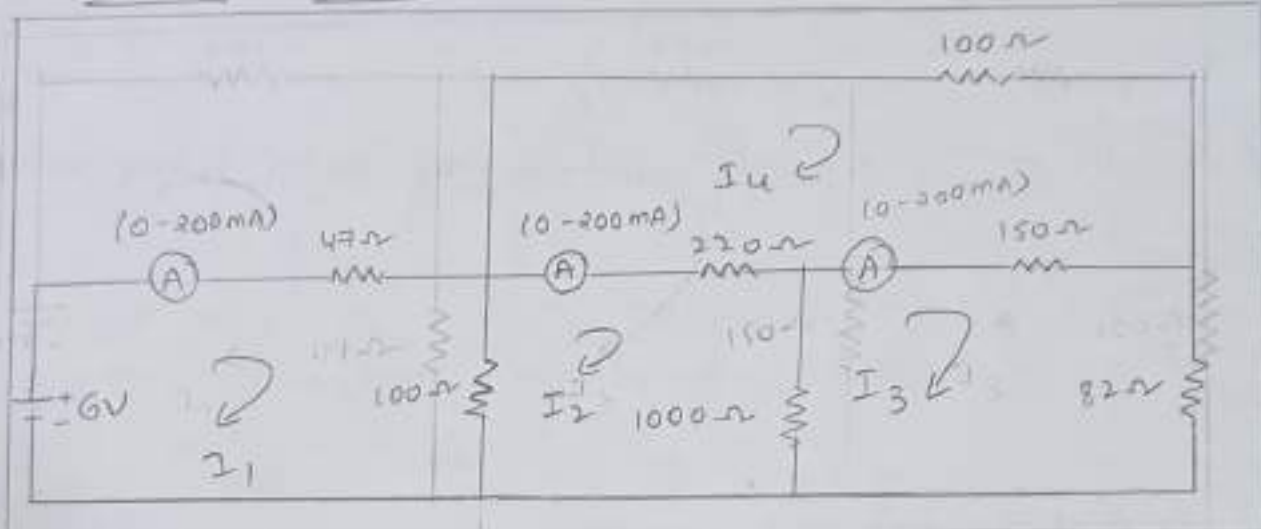Theoretical Diagram:Theoretical Calculations:

Apply KVL in Mesh-I

$$6 - 47 I_1 - 100(I_1 - I_2) = 0$$

$$147 I_1 - 100 I_2 = 6 \quad \text{--- (1)}$$

Apply KVL in Mesh-II

$$-220(I_2 - I_4) - 1000(I_2 - I_3) - 100(I_2 - I_1) = 0$$

$$100 I_1 - 1320 I_2 + 1000 I_3 + 220 I_4 = 0 \quad \text{--- (2)}$$

Apply KVL in Mesh-III

$$-82 I_3 - 1000(I_3 - I_2) - 150(I_3 - I_4) = 0$$

$$1000 I_2 - 1232 I_3 + 150 I_4 = 0 \quad \text{--- (3)}$$

Apply KVL in Mesh-IV

$$-100 I_4 - 150(I_4 - I_3) - 220(I_4 - I_2) = 0$$

$$220 I_2 + 150 I_3 - 470 I_4 = 0 \quad \text{--- (4)}$$

Solving (1), (2), (3) and (4) equations, we get:

$$I_1 = 0.03864 \text{ A} = 38.64 \text{ mA}$$

$$I_2 = 0.00203 \text{ A} = 2 \text{ mA}$$

$$I_3 = 0.0017 \text{ A} = 1.7 \text{ mA}$$

$$I_4 = 0.3629 \text{ A} = 362.9 \text{ mA}$$

Observations :-

Applied voltage 'V' (volts)	Loop current (I_1)		loop current (I_2)		loop P current (I_3)	
	Theoretical	practical	Theoretical	practical	Theoretical	practical
6 V	38.64 mA	56.7 mA	2 mA	5.5 mA	1.7 mA	3.4 mA

Precautions :-

- ① Check for proper connections before switching ON the supply.
- ② Make sure of proper colour coding of resistors.
- ③ The terminal of the resistance should be properly connected.

Result :- $\sum V_k = 0$

Mesh analysis is verified both theoretically and practically.