

**IARE****INSTITUTE OF
AERONAUTICAL ENGINEERING**(An Autonomous Institute affiliated to JNTU, Hyderabad)
Dundigal, Hyderabad - 500 043**LABORATORY WORK SHEET**Name of the Student: MADKI SAI CHARANClass: CSM-1C Semester: IstCourse Code: AEED03 Course Name: Electrical and Electronics Engineering LaboratoryName of the Course Faculty: MS M VARALAKSHMI Faculty ID: IARE 11072Exercise Number: 11 Week Number: 11 Date: 19 January 2024**DAY TO DAY EVALUATION:**

Marks	Aim / Preparation	Algorithm / Procedure	Source Code	Program Execution	Viva - Voce	Total
		Performance in the Lab	Calculations and Graphs	Results and Error Analysis		
Max. Marks	4	4	4	4	4	20
Obtained	4	4	4	4	4	20

Signature of Faculty




START WRITING FROM HERE :

Aim: plot the V-I characteristics of a Zener diode, find Zener breakdown voltage in reverse bias condition, find static and Dynamic resistance in both forward and reverse bias conditions and perform Zener diode voltage regulator.


Apparatus:

S.No	DEVICES	RANGE/ RATING	QUANTITY
01.	Zener diode trainer Board containing		
	a) DC power supply	0-15V	01
	b) Zener diode	4.7V	01
	c) Zener diode	6.2V	01
02.	d) Carbon film resistor	1K- Ω , 1/2 W	01
	DC voltmeter	0-1V	01
03.	DC voltmeter	0-20V	01
	DC Ammeter	0-200 μ A	01
04.	DC Ammeter	0-20 mA	01
	Connecting wires	5A	10

Circuit Diagram:

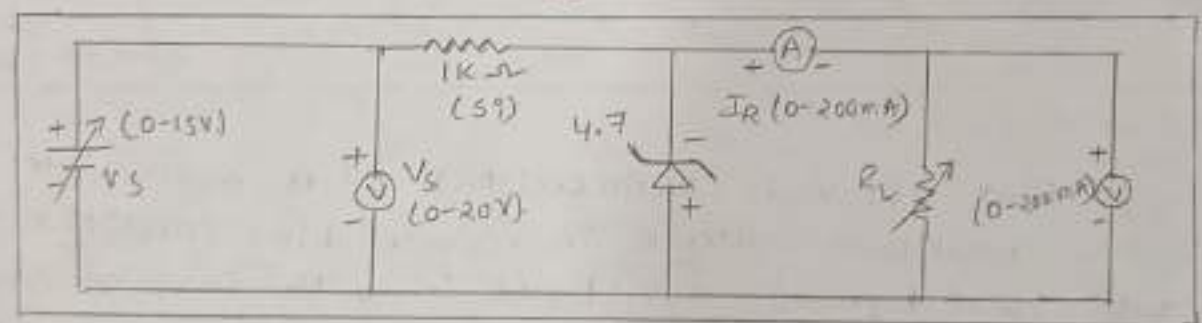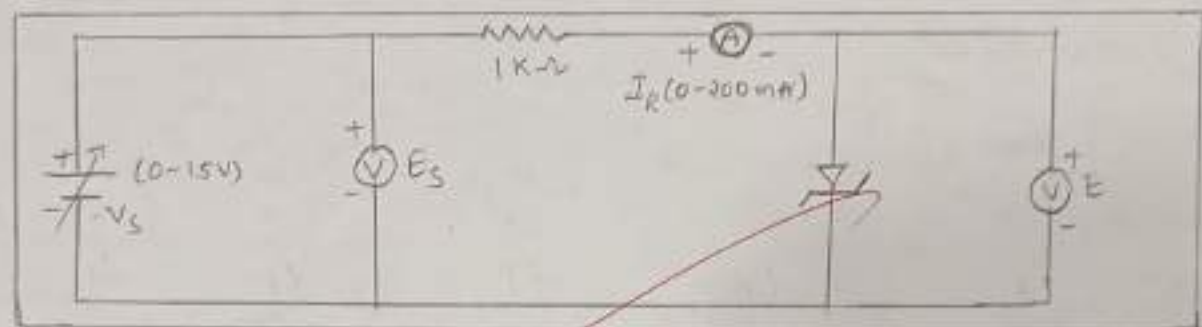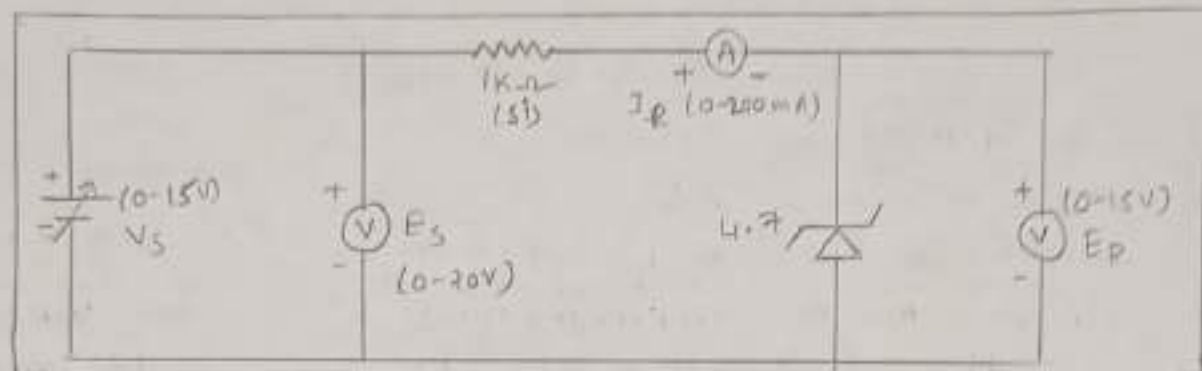

Expected graph:

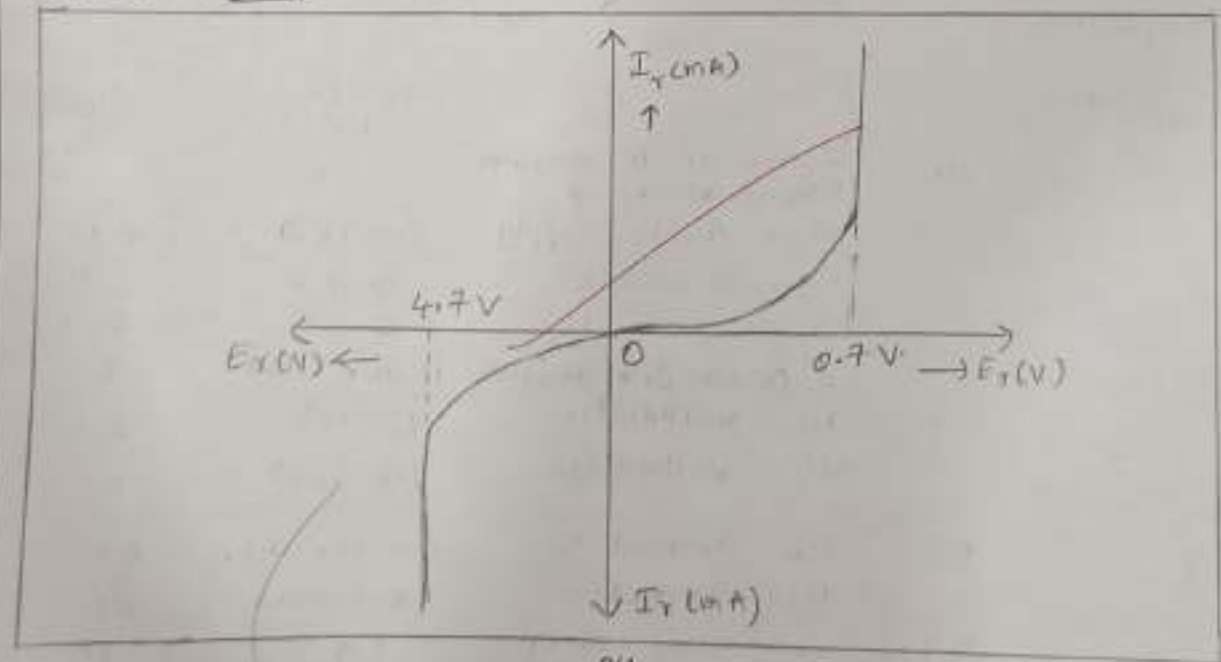

Procedure:

Forward Bias

- 1) Connect the circuit as shown in figure 1.
- 2) Vary the supply voltage E_s in steps and note down the corresponding values of E_f and I_f as shown in table.

Reverse Bias

- 1) Connect the circuit as shown in figure 2.
- 2) Repeat the procedure as in forward bias and note down the corresponding values of E_r and I_r as shown in table.

Precautions:

- 1) Ensure that polarities of power supply and meters as per circuit.
- 2) Keep the input voltage knob of regulated power supply in minimum position both when switching ON or OFF the supply.
- 3) No loose contacts at the junction.
- 4) Ensure that the ratings of meters are as per the circuit design for precision.

Result:

- 1) V-I characteristics of Zener diode are plotted and verified in both forward and reverse directions.
- 2) Zener breakdown voltage for 4.7V Zener diode = 4.7V.

3) (i) Forward Bias:

a) static resistance at 6mA =

b) Dynamic resistance at 6mA =

(ii) Reverse Bias:

a) static resistance at 6mA =

b) Dynamic resistance at 6mA =

Tabular Column:

Forward		
$E_s (V)$	$E_f (V)$	$I_f (mA)$
0.1	0.25	0
0.5	0.61	0
1	0.7	0.4
2	0.77	1.4
4	0.90	3.3
6	1.12	5.2
8	1.14	7.1
10	1.16	9.2
12	1.21	11.3
14	1.33	13.3

Reverse		
$E_s (V)$	$E_r (V)$	$I_r (mA)$
0.1	0	0
0.5	0.58	0.5
1	1.14	1.1
2	2.10	3.1
4	3.05	5.1
6	—	—
8	—	—
10	—	—
12	—	—
14	—	—

Calculations:Forward static resistance at 6mA = E_f / I_f Forward Dynamic resistance at 6mA = $\Delta E_f / \Delta I_f$ Reverse static resistance at 6mA = E_r / I_r Reverse Dynamic resistance at 6mA = $\Delta E_r / \Delta I_r$