

LABORATORY WORK SHEET

Name of the Student: Abdul Basith Khan

Class: 1st Year (CSE-A) Semester: 1st

Course Code: AEE-D01 Course Name: EEE Laboratory

Name of the Course Faculty: Dr. L. Rajashekhara Reddy

Exercise Number: 03 Week Number: 03

Date:

DAY TO DAY EVALUATION:

Marks	Aim / Preparation	Algorithm / Procedure	Source Code	Program Execution	Viva-Voce	Total
		Performance in the Lab	Calculations and Graphs	Results and Error Analysis		
Max. Marks	4	4	4	4	4	20
Obtained	4	4	4	3	4	19

Signature of Faculty

START WRITING FROM HERE :

Mesh Analysis:-

Aim:-


The study of mesh analysis is the objective of this existence especially its usage in multi-source DC circuits, its application in finding circuit currents and voltages will be investigated.

Apparatus:-

S. No.	Equipment	Range	Type	Quantity
1.	Resistor	1K Ω , 220 Ω , 470 Ω , 100 Ω , 150 Ω , 47 Ω	Carbon	06
2.	Ammeter	0-200 mA	Digital	01
3.	RPS	(0-30V)	Digital	01
4.	Bread Board	-	-	01
5.	Connecting wires	-	-	required

Theory:-

Multi source DC circuits may be analyzed using a mesh current techniques. The process involves identifying a minimum number of small loops such that every component exists in atleast one loop. KVL is then applied to each loop. The loop currents are referred as mesh currents as each. As a result there will be a set of simultaneous equations created as unknown mesh current for each loop once the mesh currents are determined various branch currents and components derived.

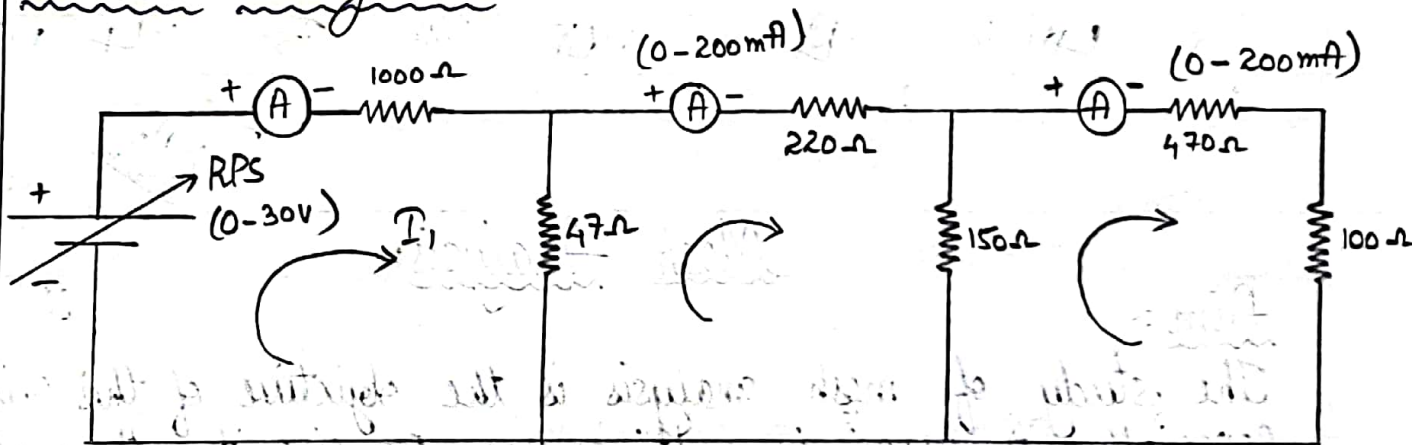Circuit Diagram:-Observation:-

Applied Voltage V (Volts)	Loop Current (I_1) mA		Loop Current (I_2) mA		Loop Current (I_3) mA	
	Theoretical	Practical	Theoretical	Practical	Theoretical	Practical
15 V	14.7	15.2	1.75	1.80	0.36	0.4

Steps:-

1. Recognize the meshes and label the diagram direction of mesh current i.e. anticlockwise or clockwise directions
2. The next step is the amount of current flowing through every circuit element is observed & noted in form of mesh.
3. Apply KVL & Ohm's law to write equations for all meshes.
4. To obtain the values of mesh currents, solve all the mesh equations obtained before.
5. Hence, the following the above steps, it is very easy to determine the current that flows through each element & the voltage that is present across the elements in circuit or network.

Procedure:-

1. Connect the circuit diagram as shown in fig.
2. Switch on the supply to RPS.
3. Apply the voltage (say 15V)
4. Gradually increase the supply voltage in steps.
5. Connect ammeters in the loop & find its current I_1, I_2, I_3
6. Verify the practical results obtained with theoretical results.

Calculations:-1st mesh:-

$$-100I_1 - 47(I_1 - I_2) + 15 = 0$$

$$-1047I_1 - 47I_2 + 15 = 0 \quad \text{--- (1)}$$

2nd mesh:-

$$-220I_2 - 150(I_2 - I_3) + 47(I_1 - I_2) = 0$$

$$47I_1 - 417I_2 + 150I_3 = 0 \quad \text{--- (2)}$$

3rd mesh :-

$$-470 I_3 - 100 I_3 + 150 (I_2 - I_3) = 0$$

$$150 I_2 - 720 I_3 = 0 \quad \text{--- (3)}$$

By Solving equations ①, ② & ③
we get

$$I_1 = 14.7 \text{ mA}$$

$$I_2 = 1.75 \text{ mA}$$

$$I_3 = 0.30 \text{ mA}$$

Precautions:-

- Check the proper connections before switching on supply
- Make sure of proper colour coding of resistors.
- The terminal of the resistance should be properly connect

Result:-

Hence, By mesh analysis, loops of voltage '0' we can find the current passing through resistance or loop easily.