



### LABORATORY WORK SHEET

Name of the Student : Abdul Basith Khan

Class : CSE (AIML) Semester : I

Course Code : ACE001 Course Name : ...

Name of the Course Faculty : Dr. L. Rajashekhar Goud Faculty ID : IARE 11067

Exercise Number : 01 Week Number : ... Date : ...

#### DAY TO DAY EVALUATION:

Marks	Aim / Preparation	Algorithm / Procedure	Source Code	Program Execution	Viva - Voce	Total
		Performance in the Lab	Calculations and Graphs	Results and Error Analysis		
Max. Marks	4	4	4	4	4	20
Obtained	4	4	4	3	4	19

Signature of Faculty

#### START WRITING FROM HERE :

AIM:-

To verify Ohm's Law for a given resistive network


APPARATUS:-

S.No	Apparatus Name	Range	Type	Quantity
1.	D.C. RPS	(0-30V)	Digital	01
2.	Ammeter	(0-200mA)	Digital	01
3.	Volt meter	(0-20V)	Digital	01
4.	Resistor	unknown	Carbon	03
5.	Bread Board	-	-	01
6.	Connecting wires	-	-	As required


THEORY:-

At constant temperature potential difference 'V' across the ends of a conductor is proportional to the current 'I' flowing through the conductor

$$V \propto I, \quad V = IR$$

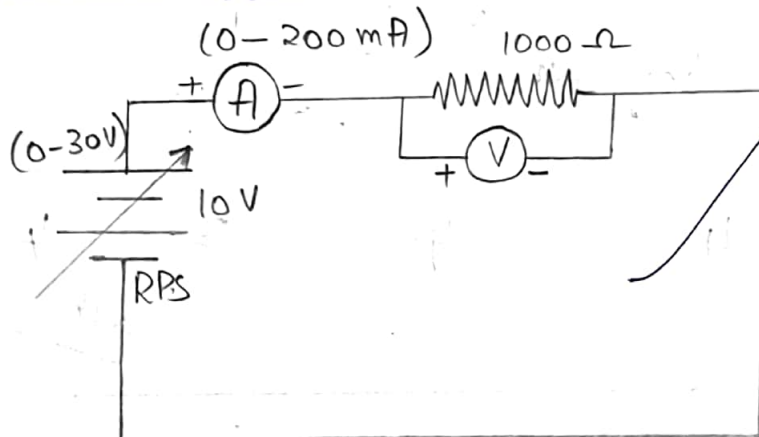CIRCUIT DIAGRAM:-OBSERVATION:-

S. No.	RPS	V, K $\Omega$ (V)		I, K $\mu$ A (mA) (A)		P (K $\Omega$ ) (W)	
		Theoretical	Practical	Theoretical	Practical	Theoretical	Practical
1.	2	2	2.19	2.1	2.1	0.004	4.818
	4	4	4.2	4.3	4.3	0.016	18.06
	6	6	6.2	0.006	6.3	0.036	39.68
	8	8	8.3	0.008	8.5	0.064	70.55
	10	10	10.3	0.01	10.7	0.1	110.21
	12	12	12.4	0.012	12.6	0.14	156.24

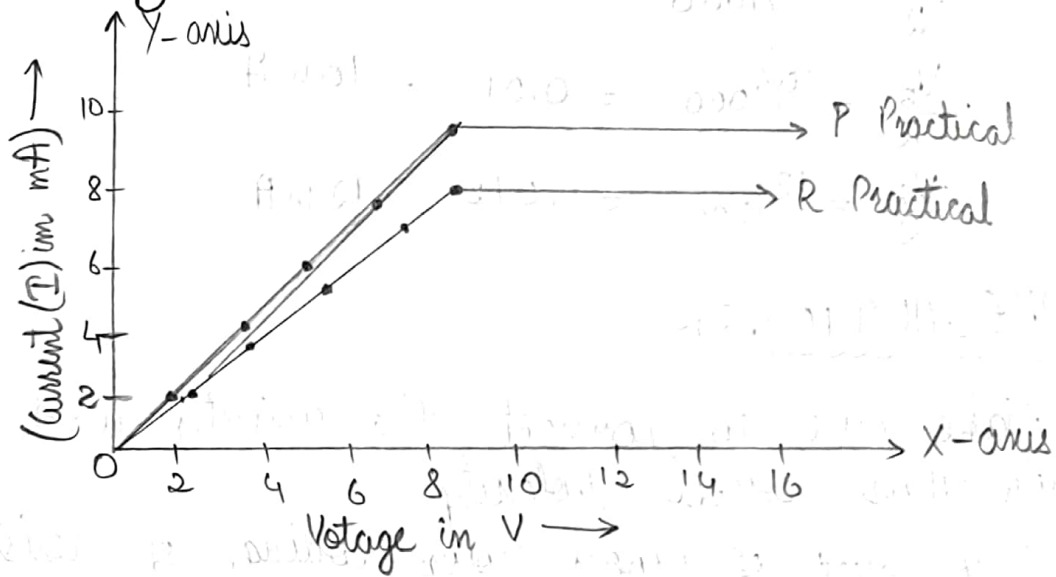MODEL GRAPH:-PROCEDURE:-

1. Make the connections as per circuit diagram.
2. Switch ON the power supply to RPS & apply a Voltage (say 10V) and take the reading of Ammeter.
3. Plot a graph with V along X-axis and I along Y-axis.
4. The graph will be a straight line which verifies the Ohm's law.
5. Determine the slope of V-I graph. The reciprocal of V-I graph gives resistance of wire.

CALCULATIONS:-

$$R = 1000 \Omega$$

$$V = IR \quad \text{SO} \quad I = V/R$$

$$\frac{V_1}{R} = 2/1000 = 0.002 = 2 \text{ mA}$$

$$\frac{V_2}{R} = 4/1000 = 0.004 = 4 \text{ mA}$$

$$\frac{V_3}{R} = 6/1000 = 0.006 = 6 \text{ mA}$$



$$\frac{V_4}{R} = 8/1000 = 0.008 = 8 \text{ mA}$$

$$\frac{V_5}{R} = 10/1000 = 0.01 = 10 \text{ mA}$$

$$\frac{V_6}{R} = 12/1000 = 0.012 = 12 \text{ mA}$$

### PRECAUTIONS:-

- \* Take care to connect the ammeter and voltmeter with their correct polarity.
- \* Make sure of proper color coding of resistors.
- \* The terminal of the resistance should be properly connected.

### RESULT:-

$$V = IR$$

Hence, Ohm's Law is verified.

### LABORATORY WORK SHEET

Name of the Student: Abdul Basith Khan  
 Class: CSE (AIML) Semester: I  
 Course Code: ACE DO1 Course Name: EEE Laboratory  
 Name of the Course Faculty: Dr L. Rajashekhar Goud Faculty ID: IARE 11067  
 Exercise Number: 01 Week Number: \_\_\_\_\_ Date: \_\_\_\_\_

Roll Number									
2	3	9	5	1	A	6	6	0	1

#### DAY TO DAY EVALUATION:

Marks	Aim / Preparation	Algorithm / Procedure	Source Code	Program Execution	Viva - Voce	Total
		Performance in the Lab	Calculations and Graphs	Results and Error Analysis		
Max. Marks	4	4	4	4	4	20
Obtained	4	4	4	3	4	19

Signature of Faculty

#### START WRITING FROM HERE :

AIM:-  
 To verify Kirchhoff's Voltage Law (KVL) & Kirchhoff's Current Law (KCL) in a positive Network


#### APPARATUS :-

S.No.	Apparatus Name	Range	Type	Quantity
1	RPS	(0-30V)	Digital	01
2	Ammeter	(0-200mA)	Digital	03
3	Volt meter	(0-20V)	Digital	03
4	Resistors	220 $\Omega$ , 150 $\Omega$ , 100 $\Omega$	Carbon	03
5	Bread Board	-	-	01
6	Connecting wires	-	-	As required

THEORY:-


KVL:- Algebraic sum of all voltages around a closed path or closed loop is Zero  $\sum V = 0$

KCL:- Sum of current flowing in the loop is equal to current leaving the loop.

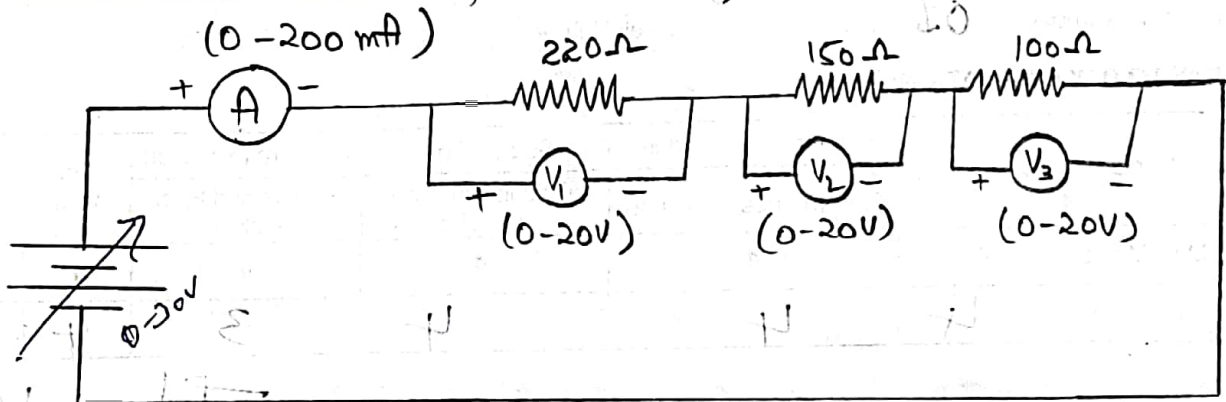PRACTICAL KVL CIRCUIT DIAGRAM:-

Supply Voltage  $V_s = I =$

S.No.	Resistor ( $\Omega$ )	Theoretical Voltage = 10V	Practical Voltage (V) = 10V
1.	220	4.60 V	4.1
2.	150	3.18 V	3.1
	100	2.12 V	2.17
3.	Total Voltage	9.96 V	9.26

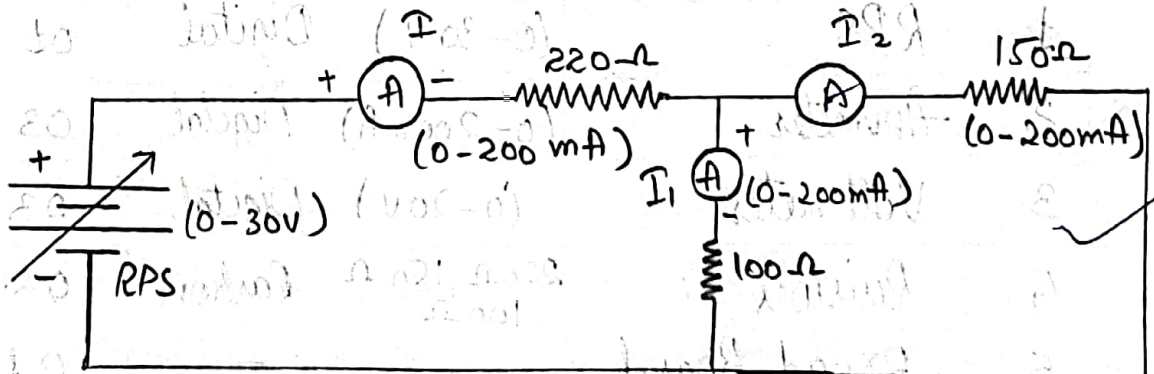PRACTICAL KCL CIRCUIT DIAGRAM:-OBSERVATIONS:-



Applied Voltage = (Volts)	$I$ (A)		$I_1$ (A)		$I_2$ (A)		$I_1 + I_2$ (A)	
	Theoretical	Practical	Theoretical	Practical	Theoretical	Practical	Theoretical	Practical
10 V	35.7 mA	36.4 mA	27.42 mA	21.3 A	14.28 mA	14.3 mA	37.5 mA	36.1 mA

### PROCEDURE :-

To verify KVL:-

- \* Connect the circuit diagram as said in the figure
- \* Switch ON the supply to RPS
- \* Apply Voltage (say 10V) & note the voltage readings
- \* Gradually increase the supply voltage in steps
- \* Note the readings of Voltmeter
- \* Sum up the voltmeter readings (voltage drops) that should be equal to applied voltage.
- \* Thus, KVL is verified practically.

To verify KCL:-

- \* Connect the circuit diagram as shown in figure
- \* Switch ON the supply to RPS
- \* Apply the voltage (say 10V) & note the ammeter readings
- \* Gradually increase the supply voltage in steps.
- \* Note the readings of ammeter.
- \* Sum up the ammeter readings ( $I_1$  &  $I_2$ ), that should be equal to total current ( $I$ ).
- \* Thus, KCL is verified Successfully practically.

### Calculation:-

## Theoretical Calculation for KVL

$$I = \frac{V}{R} = \frac{10}{4.70} = \frac{1}{4.7}$$

$$I = 0.0212 \text{ A}$$

$$V_1 = IR_1 = 0.0212 \times 220 \Rightarrow V_1 = 4.664 \text{ V}$$

$$V_2 = IR_2 = 0.0212 \times 150 \Rightarrow V_2 = 3.18 \text{ V}$$

$$V_3 = IR_3 = 0.0212 \times 100 \Rightarrow V_3 = 2.12 \text{ V}$$

$$V = V_1 + V_2 + V_3$$

$$V = 9.964$$

## Theoretical Calculation KCL

$$I = V/R = 10/280 = 0.0357 \Rightarrow = 35.7 \text{ mA}$$

$$I = 10/280 = 35.7 \text{ mA}$$

$$I_1 = I \left[ \frac{180}{150+100} \right] = \frac{35.7 \times 10^{-3} \times 150}{250} = 21.42 \text{ mA}$$

$$I_2 = \frac{100}{100+150} = \frac{35.7 \times 10^{-3} \times 100}{250} = 14.28 \text{ mA}$$

By using current division,

$$R_{eq} = \frac{150}{100} + 220$$

$$= 60 + 220$$

$$= 280 \Omega$$

Result :-

Hence, Kirchhoff's Voltage law (KVL) and Kirchhoff's Current law (KCL) is verified