

PART - A CIE (F)

M-3

- Q) A 25 kW, 250 V DC shunt generator has armature field resistance of 0.06Ω and 100Ω respectively. Determine the total armature power delivered when working
1) As generator delivering 25 kW output.

sol) Armature current; $I_a = I_L + I_{sh}$
load current; $I_L = P_L / V$

$$P_L = 25 \text{ kW}$$

$$V = 250 \text{ V}$$

$$R_a = 0.06 \Omega$$

$$R_{sh} = 100 \Omega$$

$$\therefore I_L = \frac{25000}{250}$$

$$I_L = 100 \text{ A}$$

$$\text{Shunt field current; } I_{sh} = \frac{V}{R_{sh}} = \frac{250}{100} \\ = 2.5 \text{ A}$$

$$\therefore I_a = I_L + I_{sh} = 100 + 2.5 \\ = 102.5 \text{ A}$$

$$\text{Induced voltage in armature } (E_g) = V + I_a R_a$$

$$E_g = 250 + 102.5(0.06)$$

$$E_g = 256.15 \text{ V}$$

$$\text{Power delivered; } P = E_g I_a = 256.15 \times 102.5$$

$$\boxed{P = 26225 \text{ kW}}$$

② A 8 pole DC shunt generator with 778 wave armature conductors and running at 500 rpm. supplies a load of 12.5 ohm resistance at terminal voltage of 250 volts. The armature resistance is 0.24Ω and the field resistance is 250Ω . Find the (i) armature current (ii) Induced EMF (iii) flux per pole.

Sol $Z = 778$; $N = 500 \text{ rpm}$; $R_a = 0.24 \Omega$; $R_L = 12.5 \Omega$; $R_{sh} = 250 \Omega$

(i) $I_a = ?$; $I_L = \frac{V}{R_{sh}} = \frac{250}{250} = 1 \text{ A}$;

$$I_L = \frac{V}{R_L} = \frac{250}{12.5} = 20 \text{ A}$$

$$I_a = I_L + I_{sh} = 20 + 1 \Rightarrow \boxed{I_a = 21 \text{ A}}$$

(ii) $E_g = ?$; $E_g = V + I_a R_a$

$$E_g = 250 + 21(0.24)$$

$$\boxed{E_g = 255.04 \text{ V}}$$

$P = 2$
(wave winding)

(iii) $\phi / \text{pole} = ?$; $E_g = \frac{\phi P Z N}{60 A} \Rightarrow \phi = \frac{E_g \times 60 \times A}{P \times Z \times N}$

$$\phi = \frac{255.04 \times 60 \times 2}{8 \times 778 \times 560}$$

$$\boxed{\phi = 0.00983 \text{ Wb} = 9.83 \text{ mWb}}$$

- ③ A 4 pole DC generator having wave ^{wound} armature has 50 slots and 25 conductors per slot. Find the generated EMF, if it is driven at 25 rpm & useful flux per pole in the machine is 0.03 Wb?

Sol: $P=4$; $\phi = 0.03 \text{ Wb}$; $A=2$ (wave winding); $N=25$

Total conductors = No. of slots \times conductors per slot

$$Z = 50 \times 25$$

$$Z = 1250 \quad ; \quad E_g = ?$$

$$E_g = \frac{\phi P Z N}{60 A} = \frac{0.03 \times 1250 \times 4 \times 25}{60 \times 2}$$

$$\boxed{E_g = 31.25 \text{ V}}$$

- ④ A 220V DC machine supplies 20A at 220V as a Generator. the armature resistance is 0.2 ohms. If the machine is now operated as a motor at the same terminal voltage and current but with flux increased by 10 percentage, calculate the ratio of motor speed to generator speed.

Given;

Sol (i) DC Generator; $R_a = 0.2$

$$V = 220 \text{ V}$$

(ii) DC Motor; $R_a = 0.2$

$$V = 220 \text{ V}$$

Find $\frac{N_2}{N_1} = ?$

Flux increased in motor by 10% compared to Generator

$$\phi_2 = 1.1 \phi_1$$

How? Flux of Generator Assume = 100%.

Flux of motor = 110 %

$$\phi_2 = 1.1 \phi_1$$

→ In case of Generator,

E_g = Terminal voltage + voltage drop

$$E_g = V_t + I_a R_a$$

$$E_g = 200 + 20(0.2) = 204 \text{ V}$$

→ In case of motor,

$$E_b = V_t - I_a R_a$$

$$E_b = 200 - (0.2) 20 = 196 \text{ V}$$

Turns ratio : $\frac{N_2}{N_1} = \frac{E_2}{E_1} \times \frac{\phi_2}{\phi_1}$ [$E = N\phi$]

$$\frac{N_2}{N_1} = \frac{196}{204} \times \frac{1.1 \phi_1}{\phi_1}$$

$$\boxed{\frac{N_2}{N_1} = 0.87}$$

- ⑤ A 440V DC shunt motor takes a no load current of 2.5 A. The resistance of shunt field and the armature are 550 Ω and 1.2 Ω respectively. The full load line current is 32 A. Find the full load output and the efficiency of the motor.

So 440V; $I_{\text{No load}} = 2.5 \text{ A}$; $R_{\text{sh}} = 550 \Omega$; $R_a = 1.2 \Omega$

$I_{\text{Full load}} = 32 \text{ A}$; o/p & Efficiency = ?

Input power = Voltage \times $I_{\text{full load}}$

$$\Rightarrow 440 \times 32 = 14080 \text{ W}$$

Output power = voltage \times $I_{\text{full load}}$

$$\Rightarrow 440 \times 32 = 14080 \text{ W}$$

$$\text{Efficiency} = \frac{\text{output power}}{\text{Input power}} \times 100$$

$$\eta = \frac{14080}{14080} \times 100$$

$$\boxed{\eta = 100 \%}$$

Q A three-phase, 20 hp, 208 V, 60 Hz, six pole, wye connected induction motor delivers 15 kW at a slip of 5 percent. Calculate (i) synchronous speed (ii) Rotor Speed (iii) Frequency of rotor speed

sol Given; Poles = 6; frequency = 60; slip = 5%
= 0.05

$$(i) n_s = \frac{120f}{P} = \frac{120 \times 60}{6} = 1200 \text{ rpm}$$

$$n_s = 1200 \text{ rpm}$$

$$(ii) n_r = (1-s) n_s = (1-0.05) \times 1200$$


$$n_r = 1140 \text{ rpm}$$

$$(iii) f_r = s f_s$$

$$f_r = 0.05 (60)$$

$$f_r = 3 \text{ Hz}$$

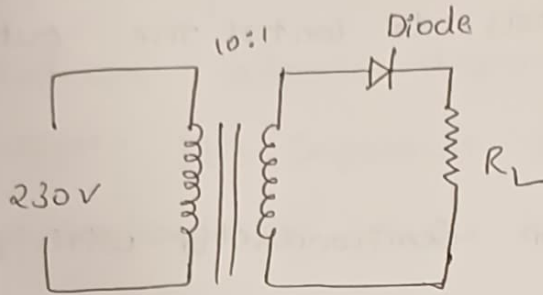- CIE-II PART-A
 Q1) An AC Supply of 230V is applied to a half wave rectifier circuit through a transformer of turn ratio 10:1. Find (i) the output dc voltage.
 (ii) The Peak inverse voltage (Assume the diode to be ideal).



Sol Given data ; $V_{rms} = 230V$ (AC Supply)

$$\text{Turns ratio} = \frac{N_1}{N_2} = 10.$$

To find (i) $V_{dc} = ?$

(ii) Peak inverse voltage.

primary to secondary turns ratio is.

RMS primary voltage = 230V

max. primary voltage is $V_{pm} = (\sqrt{2}) \times V_p (rms).$

$$\text{Note: } V_{rms} = \frac{V_m}{\sqrt{2}}$$

$$V_p (max) = \sqrt{2} \times 230 = \frac{460V}{\sqrt{2}} = 325.3V$$

$$V_m = \sqrt{2} V_{rms}$$

max. Secondary voltage is

$$V_s (max) = V_p (max) \times \frac{N_2}{N_1}$$

$$\left[\frac{V_1}{V_2} = \frac{N_1}{N_2} \right]$$

$$\Rightarrow \frac{460}{325.3} \times \frac{1}{10} = 0.1417 \times 460V$$

(i) the output d.c voltage.

(9)

$$I_{d.c} = \frac{I_m}{\pi}$$

$$V_{d.c} = \frac{I_m}{\pi} \times R_L = \frac{V_s(\max)}{\pi}$$
$$\Rightarrow \frac{32.53}{\pi} = 10.36V$$

46 14.64V

$$V_{d.c} = \frac{14.64V}{10.36V}$$

(ii) During the negative half cycle of a.c supply the reverse biased and hence conducts no current the secondary voltage appears across the diode.

$$\therefore \text{Peak Inverse voltage} = \frac{46V}{32.53V}$$

Note:

$$PIV = V_m$$

Q2) A half wave rectifier is used to supply 50V dc to a resistive load of 800Ω. The diode has a resistance of 25Ω. Calculate a.c voltage required.

Ans Given data:

$$\text{Output dc voltage } (V_{dc}) = 50V$$

$$\text{Diode resistance } r_f = 25\Omega$$

$$\text{Load resistance} = 800\Omega$$

$$\left[I_m = \frac{V_m}{r_f + R_L} \right]$$

Solution:

$$V_{dc} = I_{dc} \times R_L = \frac{I_m}{\pi} \times R_L$$

$$= \frac{V_m}{\pi(r_f + R_L)} \times R_L$$

$$50 = \frac{V_m}{\pi(25+800)} \times 800$$

$$V_m = \frac{\pi \times 25 \times 50}{800} = 162 \text{ V}$$

Hence a.c voltage of maximum value 162 V is required

Q3) A full wave rectifier uses two diodes, the internal resistance of each diode may be assumed constant at 20Ω . The transformer rms secondary voltage from centre tap to each end of secondary is 50 V and load resistance is 980Ω . Find.

(i) the mean load current

(ii) the rms value of load current.

Sol

Given data:

diode resistance, $r_f = 20 \Omega$; $R_L = 980 \Omega$, $V_{rms} = 50 \text{ V}$

$$\begin{aligned} \text{Max. AC voltage } V_m &= 50 \times \sqrt{2} \\ &= 70.7 \text{ V} \end{aligned}$$

$$\begin{aligned} \text{Max. load current } I_m &= \frac{V_m}{r_f + R_L} = \frac{70.7}{20 + 980} \\ &= 70.7 \text{ mA} \end{aligned}$$

(i) Mean load current

$$\begin{aligned} I_{d.c} &= \frac{2 I_m}{\pi} = \frac{2 \times 70.7}{\pi} \\ &= 45 \text{ mA} \end{aligned}$$

$$\boxed{I_{d.c} = 45 \text{ mA}}$$


(ii) RMS value of load current is

$$I_{rms} = \frac{I_m}{\sqrt{2}} = \frac{70.7}{\sqrt{2}} = 50 \text{ mA}$$

$$I_{rms} = 50 \text{ mA}$$

- Q4). An a.c. supply of 230V is applied to a bridge type Rectifier circuit through a transformer of turns ratio 4:1. Find (i) d.c. out voltage.
 (ii) Peak inverse voltage.
 (iii) Output frequency. Assume the diodes are ideal.

Sol

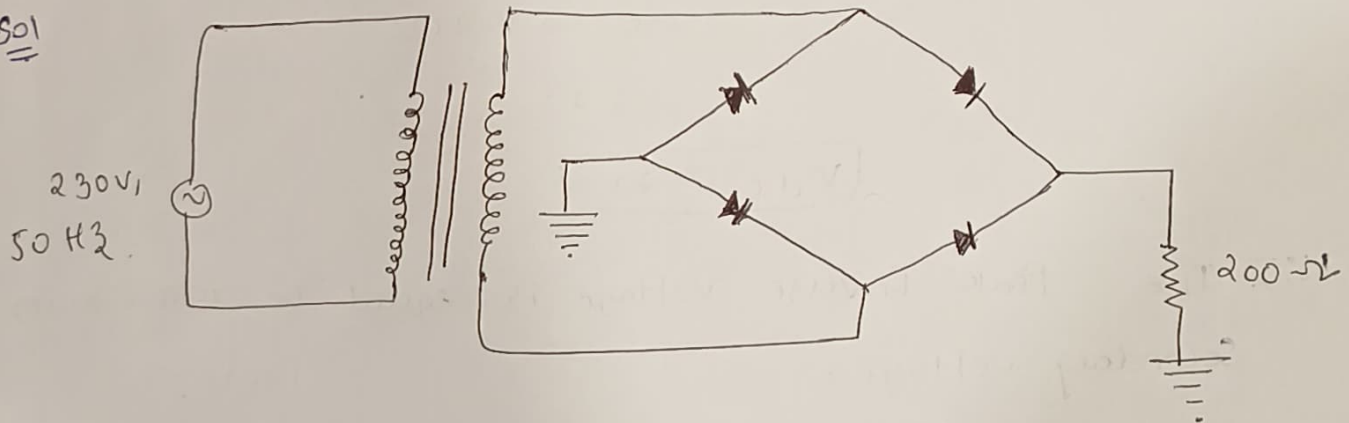

Turns ratio $\frac{N_1}{N_2} = \frac{4}{1}$

$$\frac{V_1}{V_2} = \frac{N_1}{N_2}$$

RMS Primary voltage = 230V

RMS Secondary voltage = $230 \times \frac{N_2}{N_1}$

$$= 230 \times \frac{1}{4}$$

$$= 57.5 \text{ V}$$

Maximum voltage across secondary is

$$V_{\max} = 57.5 \times \sqrt{2}$$
$$= 81.3 \text{ V}$$

$$\boxed{V_{\max} = 81.3 \text{ V}}$$

Note

$$V_{\max} = \sqrt{2} \times V_{\text{rms}}$$

(i) Average current $I_{\text{d.c}} = \frac{2 V_m}{\pi R_L}$

Note

$$I_{\text{d.c}} = \frac{2 I_m}{\pi}$$

$$I_{\text{d.c}} = \frac{2 \times 81.3}{\pi \times 200} = 0.26 \text{ A}$$

$$I_m = \frac{V_m}{R_L}$$

d.c output voltage $V_{\text{d.c}} = I_{\text{d.c}} \times R_L$

$$= 0.26 \times 200$$
$$= 52 \text{ V}$$

$$\boxed{V_{\text{d.c}} = 52 \text{ V}}$$

(ii). The Peak Inverse Voltage is equal to maximum Secondary voltage.

Note;

$$PIV = V_{\max}$$

$$\boxed{PIV = 81.3 \text{ V}}$$

(iii) In full wave rectification, there are two output pulses for each complete cycle of the input a.c. voltage.

$$f_{\text{out}} = 2 \times f_{\text{in}}$$
$$= 2 \times 50$$
$$= 100 \text{ Hz}$$

$$\boxed{f_{\text{out}} = 100 \text{ Hz}}$$

5) An half wave rectifier has a load of $3.5 \text{ K}\Omega$. If the diode resistance and secondary coil resistance together have a (ii) resistance of 800Ω and the input voltage has a signal voltage of peak value 240 . Calculate.

(a) Peak, average and rms values of current flowing.

(b) dc power output.

(c) a.c power input.

(d) efficiency of the rectifier.

Ans Given data : , $R_L = 3.5 \text{ K}\Omega$

$$R_s + R_f = 800 \Omega \text{ and } V_m = 240 \text{ V.}$$

(a) Peak value of current
$$I_m = \frac{V_m}{R_f + R_s + R_L}$$
$$= \frac{240}{800 + 3 \times 500}$$

$$I_m = 55.81 \text{ mA}$$

Average value of current
$$I_{dc} = \frac{I_m}{\pi} = \frac{55.81}{\pi}$$

$$I_{dc} = 17.77 \text{ mA}$$

Rms value of current
$$I_{rms} = I_m / 2$$

$$= \frac{55.81 \times 10^{-3}}{2}$$

$$= 27.9 \text{ mA}$$

$$I_{rms} = 27.9 \text{ mA}$$

(b) d.c power output

$$P_{dc} = I_{dc}^2 R_L$$

$$= (7.77 \times 10^{-3})^2 \times 3500$$

$$= 1.105 \text{ W}$$

$$\boxed{P_{dc} = 1.105 \text{ W}}$$

(c) A.c Input power

$$P_{AC} = I_{rms}^2 \times (R_f + R_L + R_s)$$

$$= (27.905 \times 10^{-3})^2 \times (3500 + 800)$$

$$= (27.9 \times 10^{-3})^2 \times 4300$$

$$\boxed{P_{AC} = 3.348 \text{ W}}$$

(d) Efficiency. $(\eta) = \frac{P_{d.c}}{P_{a.c}}$

$$\eta = \frac{1.105}{3.348} \times 100$$

$$\boxed{\eta = 33\%}$$

— THE

END —