

LABORATORY WORK SHEET

Name of the Student : Abdul Basith Khan
 Class : 1st Year (CSM-A) Semester : 1st
 Course Code : AEE001 Course Name : EEE laboratory
 Name of the Course Faculty : Dr. L. Rajashekhara Goud Faculty ID : IARE11067
 Exercise Number : 12 Week Number : 12 Date : 22/01/2024

DAY TO DAY EVALUATION:

Marks	Aim / Preparation	Algorithm / Procedure	Source Code	Program Execution	Viva - Voce	Total
		Performance in the Lab	Calculations and Graphs	Results and Error Analysis		
Max. Marks	4	4	4	4	4	20
Obtained	4	4	4	4	4	20

Dr. L. Rajashekhara Goud
Signature of Faculty

START WRITING FROM HERE : HALF WAVE RECTIFIER WITH/WITHOUT

Aim:- Examine the input and output wave forms of a half wave rectifier without and with filters. Calculate the ripple factor of 500 Ω , 1K Ω . & 10K Ω respectively. Calculate ripple factor with a filter capacitor of 100 μ F and the load of 1K Ω , 2K Ω . & 10K Ω respectively.

Apparatus Required:-

S.No.	Device	Range	Quantity in No.
1.	Rectifier and Filter trainer Board containing a) AC Supply b) Silicon Diodes c) Capacitor	(12-0-12)V 1N4007 100 μ F	1 1 1
2.	a) DC Voltmeter b) AC Voltmeter	(0-20)V 1/4 (0-20)V	1 1

3.	DC Ammeter	(0-200) mA	1
4.	Cathode Ray	(0-20) mHz	1
5.	Decode Resistance Box	10 Ω - 10 k Ω	1
6.	Connecting Wires	5A	12

Circuit Diagram:-

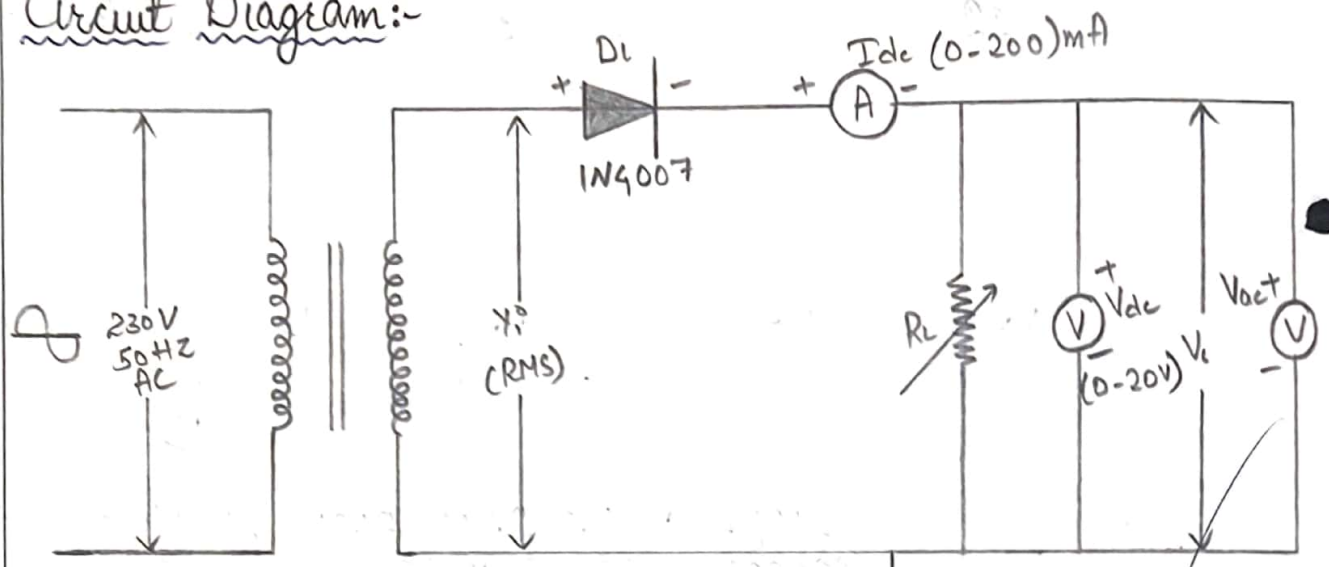


Fig-12.1 Half wave Rectifier Without Filter.

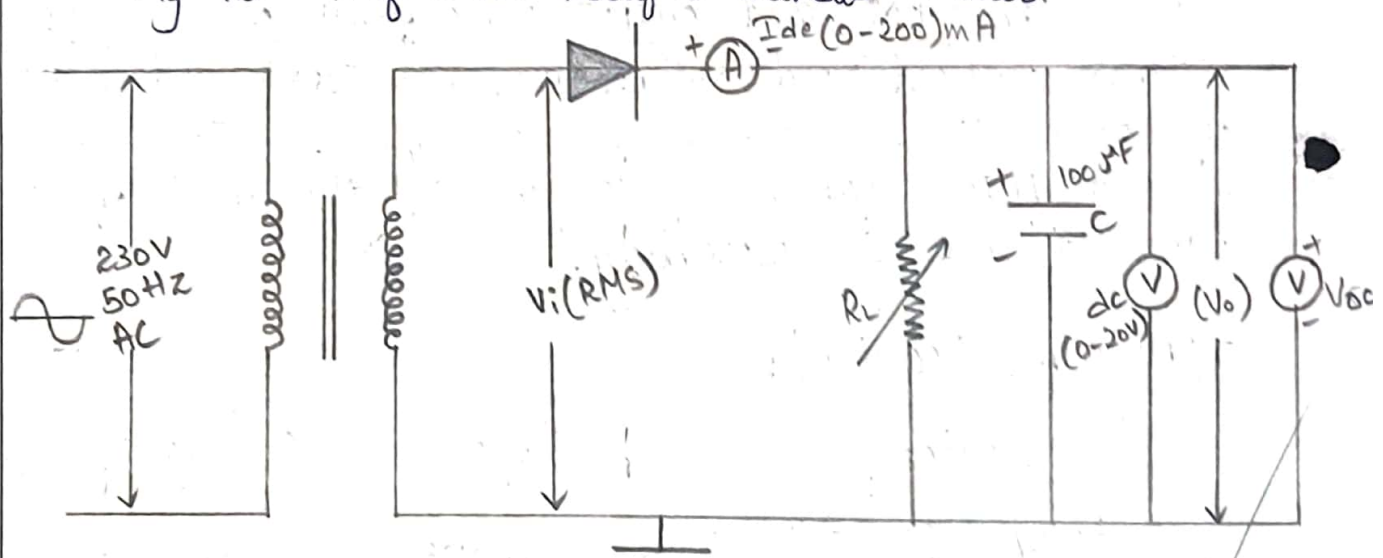


Fig 10.2 Half wave Rectifier with filter.

Procedure:-


* Half Wave rectifier without filter:-

1. Connect the circuit as shown in Fig-10.1
2. Adjust the load resistance to $R_L 500\Omega$ and note down the readings of input and output voltages through Oscilloscope
3. Note the readings of DC current, DC voltages and AC Voltage.
4. Now change the load resistance R_L to $1K\Omega$ and repeat the procedure as above. Also repeat for $1K\Omega$
5. Readings are tabulated as per the tabular column.

*Half Wave Rectifier With filter:-

1. Connect the circuit as shown in fig-10.2 and repeat the procedure as for half wave rectifier without filter.

Expected graphs:-

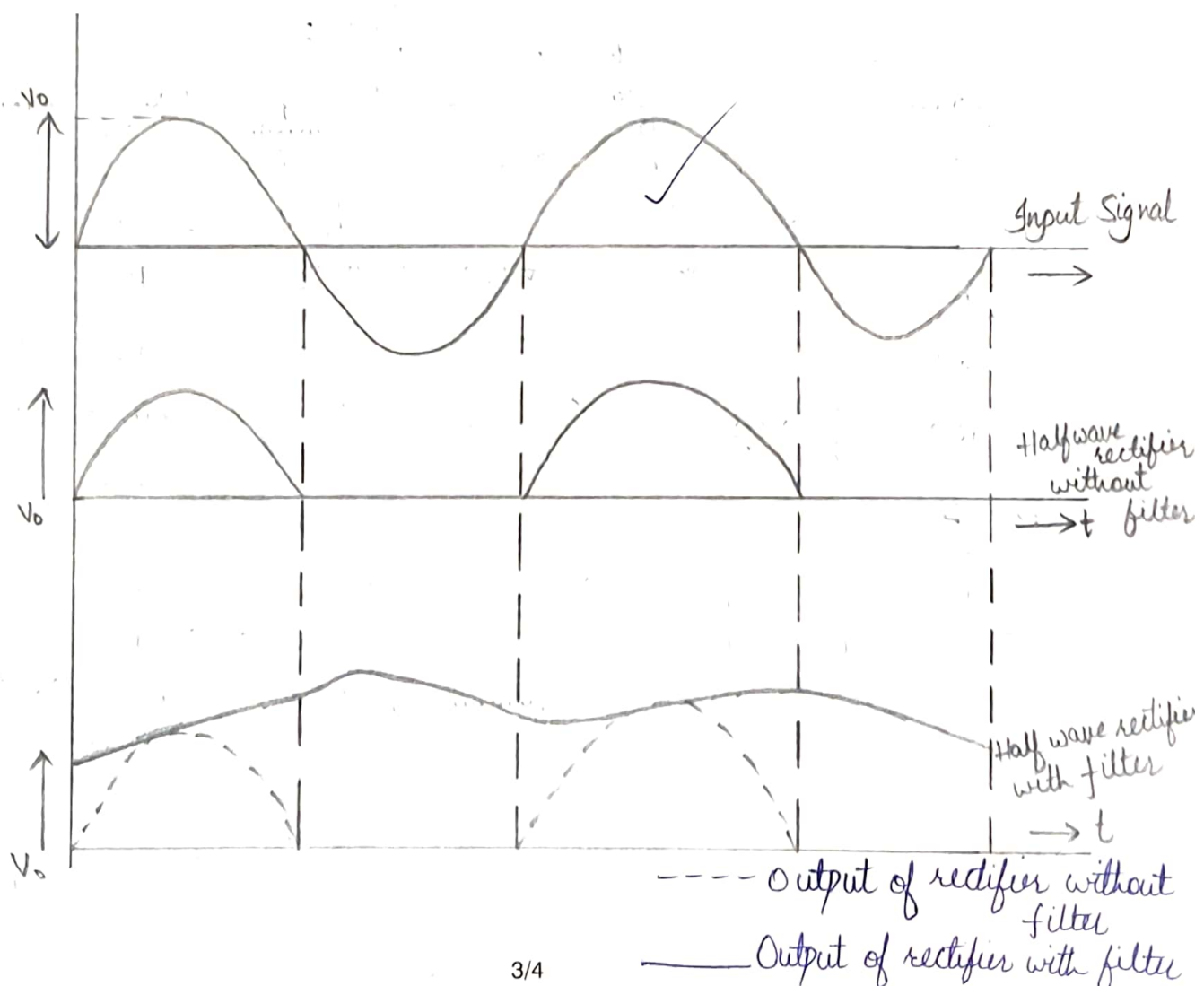

Precautions:-

1. No loose contacts at the junctions.
2. Meters of correct range must be use for precision.

Tabular Columns:-Half wave rectifier without filter:-

S.No	Load Resistance (R_L) Ω	Input Voltage Peak (V_m)	Output Voltage Peak (V_o)	Average DC Current (I_{dc}) (A)	Average DC Voltage (V_{dc}) (V)	RMS Voltage (V_{ac})	Ripple factor $\gamma = V_{ac}/V_{dc}$
1.	100 Ω	18.00	16.40	49.8	4.93	6.19	1.24
2.	220 Ω	20.00	18.40	26.0	5.48	6.90	1.25
3.	470 Ω	20.40	20.00	12.2	5.76	7.06	1.22
4.	1000 Ω	20.80	20.00	5.9	5.90	7.47	1.26

Half wave rectifier with filter:-

S.No	Load Resistance (R_L) Ω	Input Voltage Peak (V_m)	Output Voltage Peak (V_o)	Average DC Current (I_{dc}) (A)	Average DC Voltage (V_{dc}) (V)	RMS Voltage (V_{ac})	Ripple factor $\gamma = V_{ac}/V_{dc}$
1.	100 Ω	16.40	15.60	19.2	7.78	3.64	0.46
2.	220 Ω	18.00	16.80	51.3	11.20	2.70	0.24
3.	470 Ω	18.80	18.00	30.3	14.1	1.55	0.09
4.	100 Ω	20.00	18.00	16.4	16.3	0.14	8.58

Result:-

1. Input and output wave forms of a half-wave rectifier with/without filter are observed and plotted.
2. For half wave rectifier without filter - γ Ripple factor
 - 470 Ω = 1.22
 - 100 Ω = 1.24
 - 220 Ω = 1.25
3. For half wave rectifier with filter - γ Ripple factor at
 - 200k Ω , 100 μF = 0.24
 - 100 K Ω , 100 μF = 8.58

