

## LABORATORY WORK SHEET

Name of the Student : Abdul Basith Khan  
 Class : 1<sup>st</sup> Year (CSM-A) Semester : I<sup>st</sup>  
 Course Code : AEED01 Course Name : EEE Laboratory  
 Name of the Course Faculty : Dr. L. Rajashekhar Goud Faculty ID : IARE11067  
 Exercise Number : 05 Week Number : 05 Date : 12/01/2024

Roll Number									
2	3	9	5	1	A	6	6	0	1

### DAY TO DAY EVALUATION:

Marks	Aim / Preparation	Algorithm / Procedure	Source Code	Program Execution	Viva - Voce	Total
		Performance in the Lab	Calculations and Graphs	Results and Error Analysis		
Max. Marks	4	4	4	4	4	20
Obtained	4	4	4	3	4	19

Signature of Faculty

### START WRITING FROM HERE :

Norton's Theorem:-

Aim:-


To verify Norton's Theorem for electrical circuit theoretically and practically.

Apparatus:-

S.No	Equipment	Range	Type	Quantity
1.	Ammeter	(0-200 mA)	Digital	1
2.	Voltmeter	(0-20)V	Digital	1
3.	RPS	(0-30)V	Digital	1
4.	Bread board	-	-	1
5.	Resistor	100 $\Omega$ , 1000 $\Omega$ 220 $\Omega$ , 150 $\Omega$	-	4
6.	Connecting wires	- 1/4	-	As Required

Statement:-

Any linear, bilateral network with current sources, voltage source and resistor can be replaced by one equivalent circuit consisting of a current source in parallel with a resistor. The value of the current source is the current flowing through the short circuit terminals of the network and the resistor is the equivalent resistance measure between the open circuit terminals of the network with all the energy sources replaced by internal resistor.

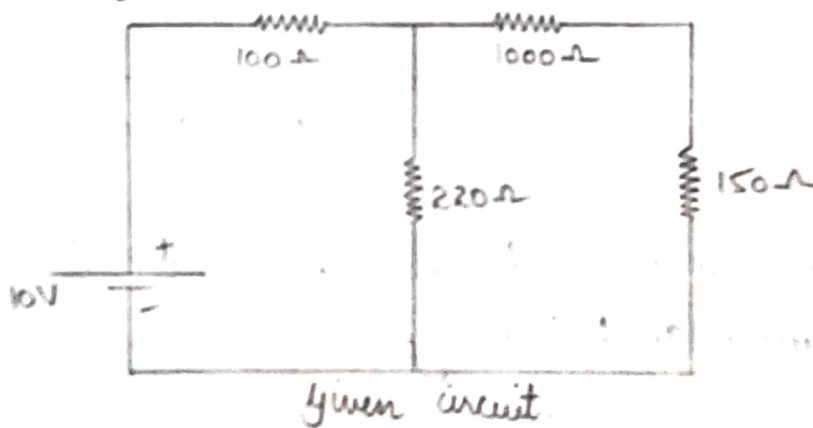Circuit Diagram:-

①

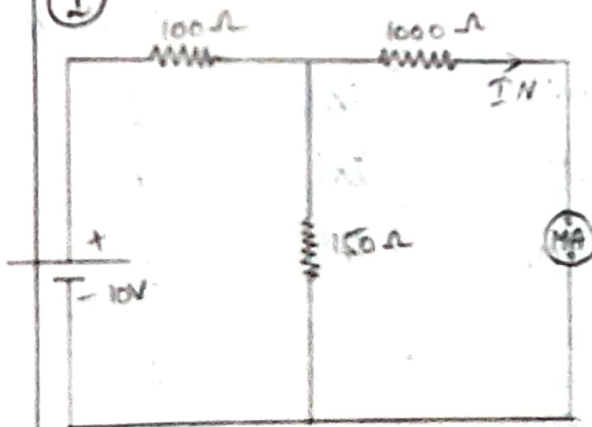


Fig (1)

②


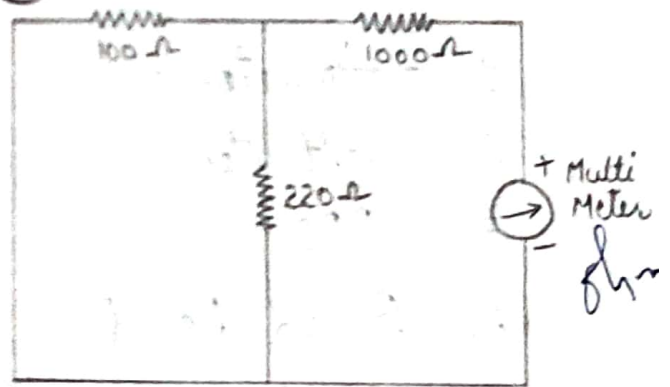


Fig (2)

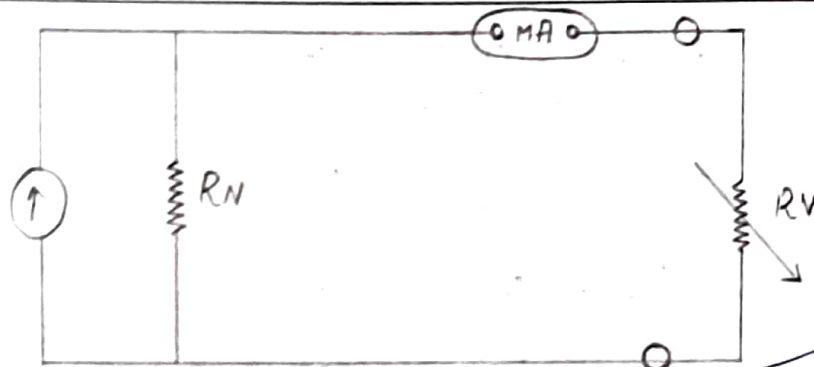

Norton Equivalent Resistance  
Fig(3)

### Procedure:-

1. Connect the circuit diagram as shown in Fig(1) and Fig(2), measure the current  $FSC$  (or)  $I_N$  through short circuited terminal
2. Find the resistance b/w open circuited terminal by using multimeter.
3. Draw Norton's Equivalent circuit by connecting  $I_N$  and  $R_N$  in parallel as shown in fig(3) and find load current.

### Tabular Column:-

Parameter	Theoretical Values	Practical Values
$FSC$ (or) $I_N$	6.311 mA ✓	7.0 mA
$R_N$	1068.75 $\Omega$ ✓	1048 $\Omega$ ✓
$I_2$	5.534 mA	6.1 mA

### Calculations:-

$$\begin{aligned}
 R_T &= \left[ \frac{1}{100} + \frac{1}{220} \right] + 100 \\
 &= \frac{1000 \times 220}{1220} + 100 \\
 &= 180.32 + 100
 \end{aligned}$$

$$R_T = 280.32 \Omega \quad 3/4$$



$$R_N = \frac{100 \times 220}{100 + 220} + 100$$

$$= \frac{22000}{320} + 100$$

$$R_N = 1068.72 \, \Omega$$

$$I_T = \frac{V}{R} = \frac{10}{280.32}$$

$$I_T = 0.035 \, A$$

$$I_N = \frac{I_T \times 220}{220 + 1000}$$

$$= \frac{0.035 \times 220}{1220}$$

$$= 0.0066 \, A$$

$$I_N = 6.311 \, mA$$

$$I_2 = 6.3 \times 1068.75$$

$$I_2 = \frac{6744.88}{1218.75}$$

$$I_2 = 5.534 \, mA$$

Result:-

Any linear circuit containing several voltages & resistance can be replaced by just one simple single current source in parallel with a single resistance connected across the load.

Conclusion:-

We can solve any example complex circuit with just a single current source and parallel resistance connected to a load.