



### LABORATORY WORK SHEET

Name of the Student: MADKI SAI CHARAN

Class: CSM-'C' Semester: I<sup>st</sup>

Course Code: AEE003 Course Name: Electrical and

Electronics Engineering Laboratory

Name of the Course Faculty: Ms. M. VARA LAKSHMI

Faculty ID: IARE11072


Exercise Number: 01

Week Number: 01

Date: 13 October 2023

#### DAY TO DAY EVALUATION:

Marks	Aim / Preparation	Algorithm / Procedure	Source Code	Program Execution	Viva - Voce	Total
		Performance in the Lab	Calculations and Graphs	Results and Error Analysis		
Max. Marks	4	4	4	4	4	20
Obtained	4	4	4	4	4	20

  
Signature of Faculty

START WRITING FROM HERE: OHM'S LAW


Aim : To verify ohm's law for a given resistive network.

Apparatus :

Serial Number	Apparatus Name	Range	Type	Quantity
01.	RPS	(0-30V)	Digital	01
02.	Ammeter	(0-200mA)	Digital	01
03.	Voltmeter	(0-30V)	Digital	01
04.	<del>Resistor</del>	unknown	Carbon	03.
05.	Bread board	-	-	01
06.	Rheostat	(0-20K)	-	01
07.	Connecting wires	-	-	As required.


Procedure :

- ① Make the connections as per circuit diagram.
- ② Switch ON the power supply to RPS and apply a voltage (say 10V) and take the reading of voltmeter and ammeter.
- ③ Adjust the rheostat in steps and take down the readings of ammeter and voltmeter.
- ④ plot a graph with 'V' along x-axis and 'I' along y-axis.
- ⑤ The graph will be a straight line which verifies ohm's law.
- ⑥ Determine the slope of the V-I graph, the reciprocal of slope gives resistance of the wire.

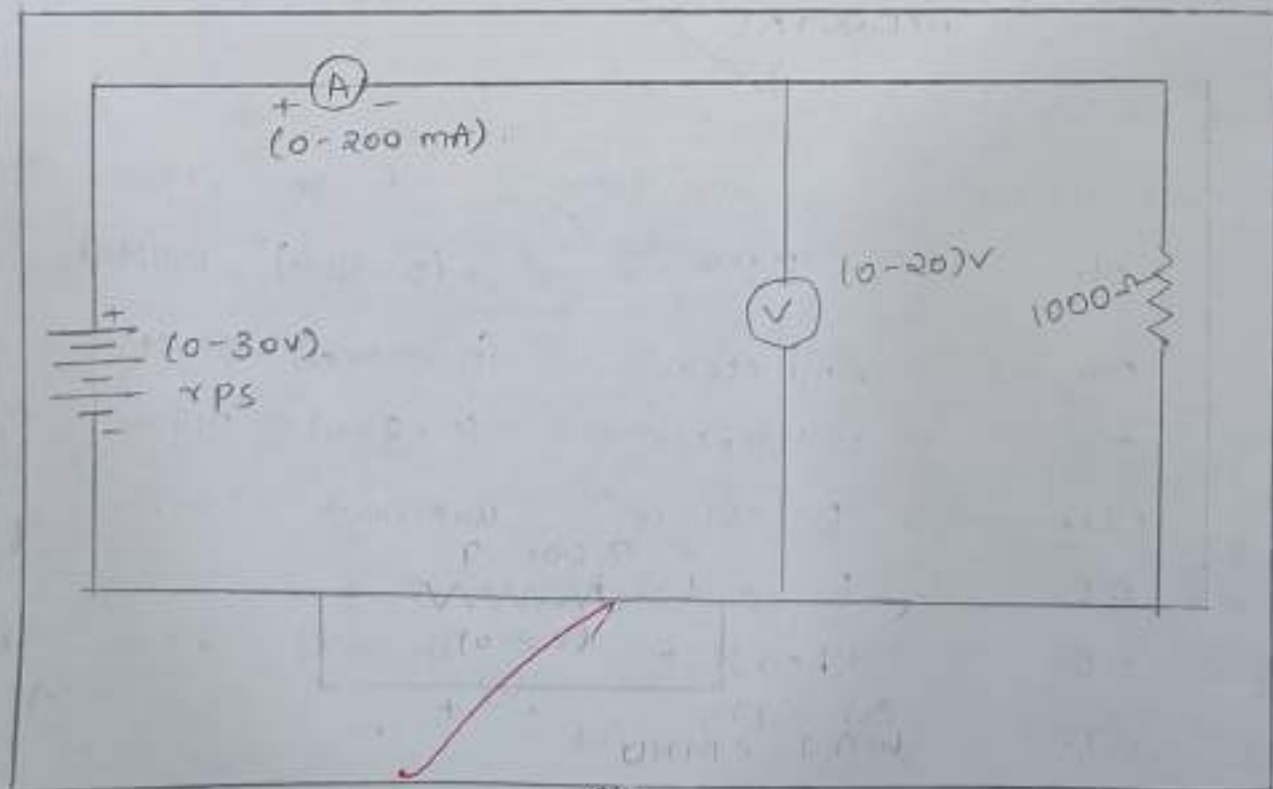Circuit Diagram:

Observations :

S.No	V <sub>Supply</sub>	I (Theoretical) (mA)	I (Practical) mA
(1)	2V	2mA	2.3 mA
(2)	4V	4mA	4.4 mA
(3)	6V	6mA	6.5 mA
(4)	8V	8mA	8.6 mA
(5)	10V	10mA	10.7 mA

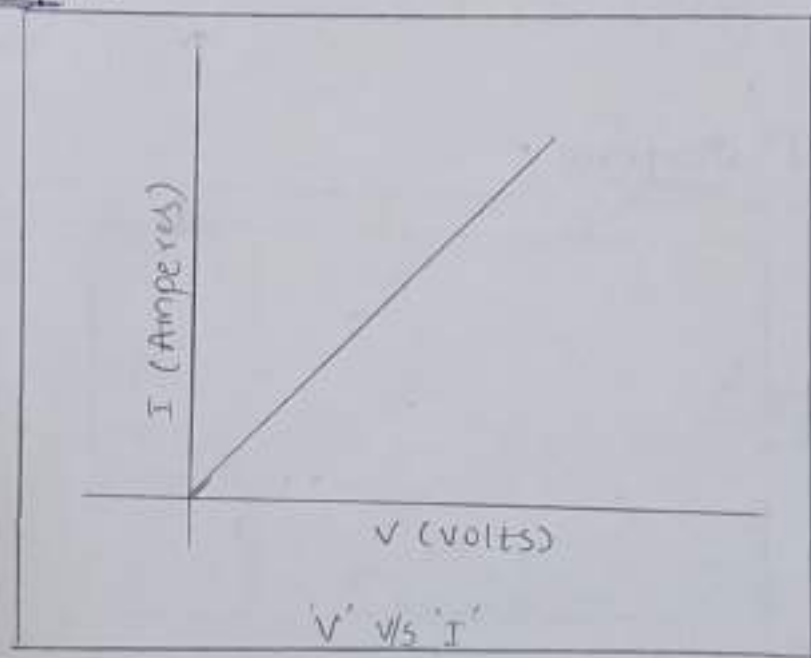Model graph :Precautions :

- ① Take care to connect the ammeter and voltmeter with their correct polarities.
- ② Make sure of proper color coding of resistors.
- ③ The terminal of the battery should be properly connected.

### Calculations:

$$V = IR \quad ; \quad \boxed{I = \frac{V}{R}}$$

$$\textcircled{1} \quad I = \frac{V_1}{R} = \frac{2}{1000} = 2 \text{ mA}$$


$$\textcircled{4} \quad I = \frac{V_4}{R} = \frac{8}{1000} = 8 \text{ mA}$$

$$\textcircled{2} \quad I = \frac{V_2}{R} = \frac{4}{1000} = 4 \text{ mA}$$

$$\textcircled{5} \quad I = \frac{V_5}{R} = \frac{10}{1000} = 10 \text{ mA}$$

$$\textcircled{3} \quad I = \frac{V_3}{R} = \frac{6}{1000} = 6 \text{ mA}$$

### Theoretical Diagram:

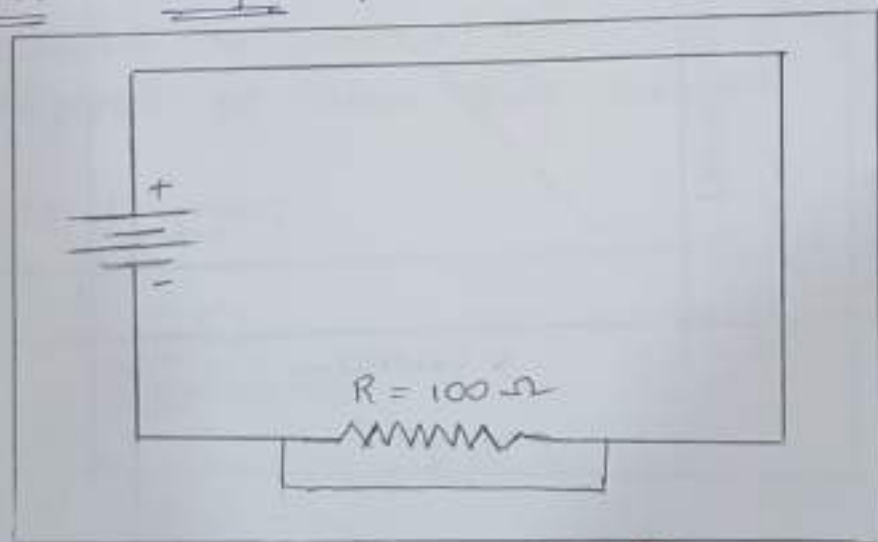


Result: Hence, Ohm's law is verified.

*Dr.*



Ohm's lawScale

On x-axis unit = 1V

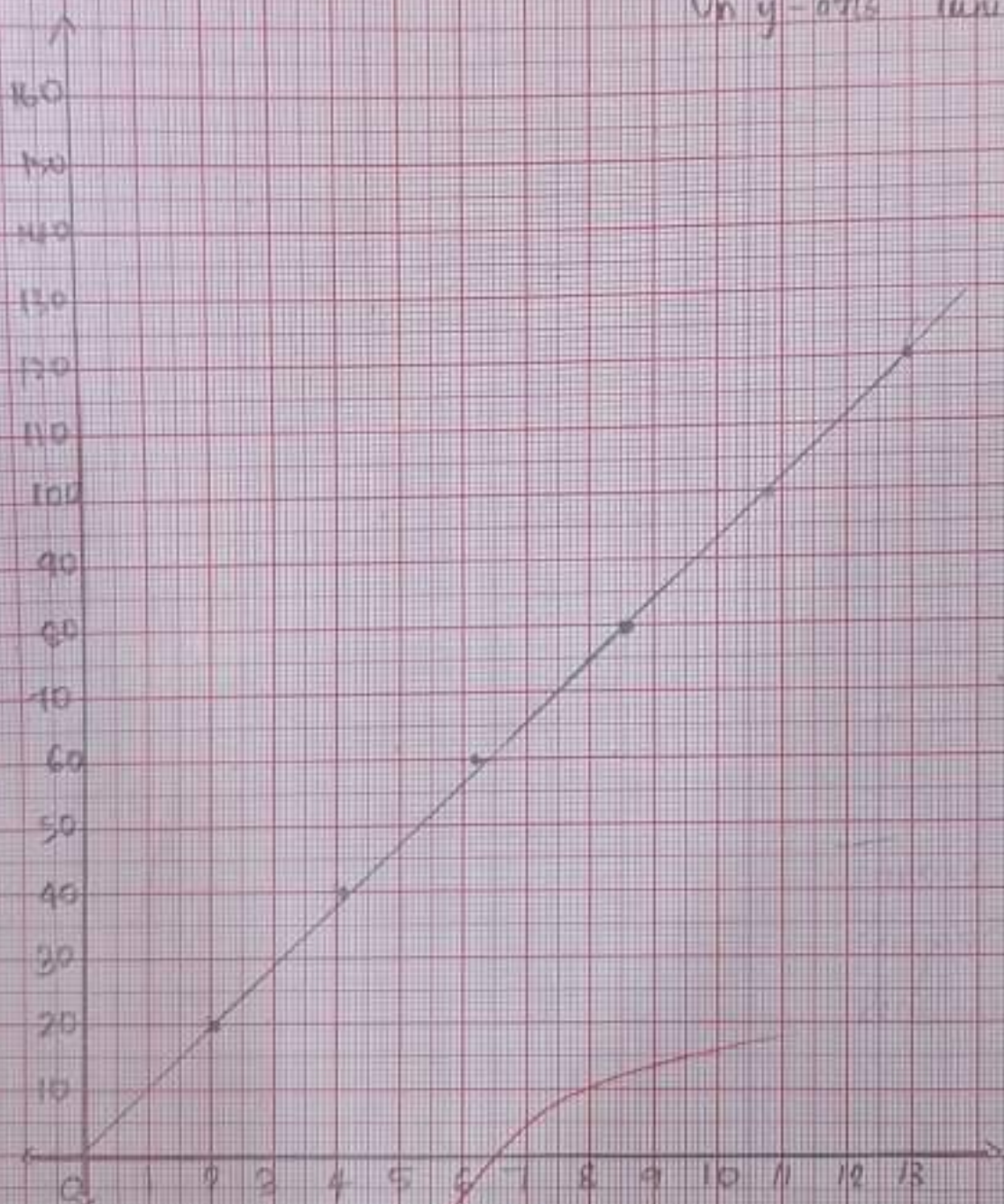On y-axis unit = 10 $\Omega$ 



## LABORATORY WORK SHEET

Name of the Student: MADKI SAI CHARAN

Class: C5M-C Semester: I<sup>st</sup>

Course Code: AEE D03 Course Name: Electrical and Electronics Engineering Laboratory

Name of the Course Faculty: MS. M. VARALAKSHMI Faculty ID: IARE 11072

Exercise Number: 01 Week Number: 01 Date: 27 October 2023

### DAY TO DAY EVALUATION:

Marks	Aim / Preparation	Algorithm / Procedure	Source Code	Program Execution	Viva - Voce	Total
		Performance in the Lab	Calculations and Graphs	Results and Error Analysis		
Max. Marks	4	4	4	4	4	20
Obtained						

Signature of Faculty

### START WRITING FROM HERE :

Aim : To verify Kirchhoff's voltage law (KVL) and Kirchhoff's current law (KCL) in a passive resistive network.

Statement :

Kirchhoff's voltage law states that "The sum of all voltages (or) potential differences in an electrical circuit loop is zero."

$$\sum_k V_k = 0$$



Kirchhoff's current law states that "The sum of all currents that enters an electrical circuit junction is zero." The currents enter the junction have positive sign and the currents that leave the junction have negative sign.

$$\sum_k I_k = 0$$



Apparatus :

S.NO	Apparatus Name	Range	Type	Quantity
01.	RPS	(0-30V)	Digital	01.
02.	Ammeter	(0-200mA)	Digital	03.
03.	Voltmeter	(0-30V)	Digital	03.
04.	Resistors	unknown	Carbon	03.
05.	Bread Board (Board)	-	-	01.
06.	Connecting Wires	-	-	As required.

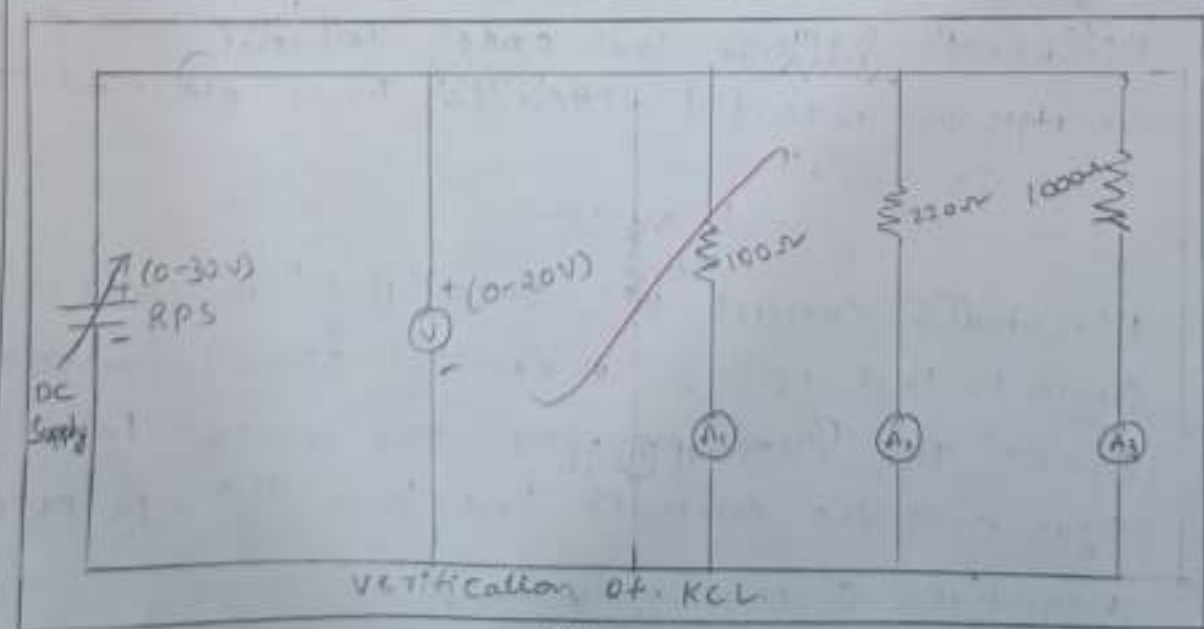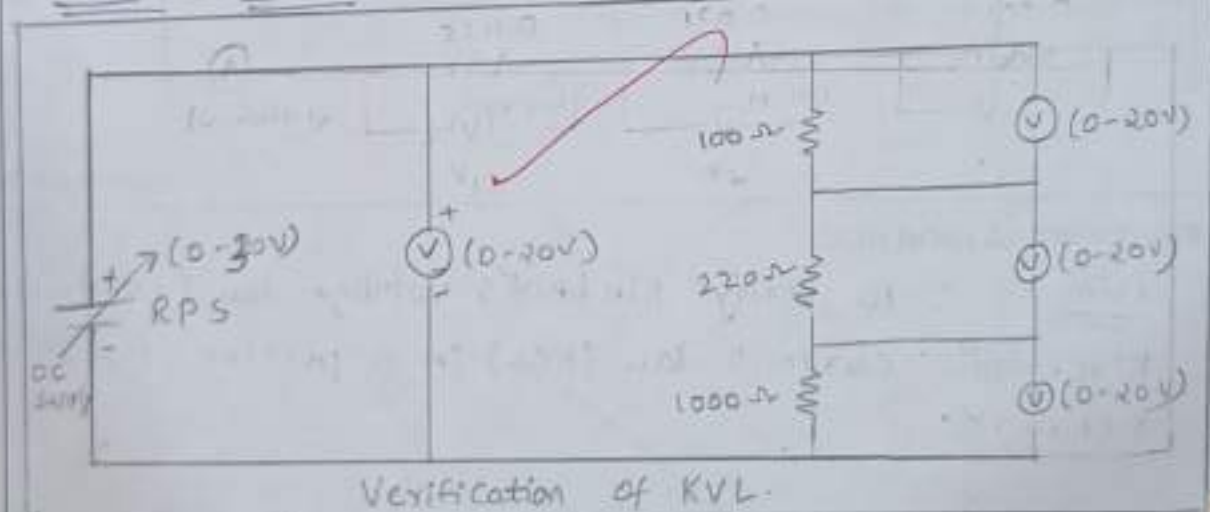Circuit Diagram:

Procedure :To verify KVL:

- ① Connect the circuit diagram as shown in fig 1.
- ② Switch ON the supply to RPS.
- ③ Apply the voltage (say 5V) and note the voltmeter readings.
- ④ Gradually increase the supply of voltage in steps.
- ⑤ Note the readings of voltmeter.
- ⑥ Sum up the voltmeter readings (voltage drops), that should be equal to applied voltage.
- ⑦ Thus KVL is verified practically.

To verify KCL:

- ① Connect the circuit diagram as shown in fig 2.
- ② Switch ON the supply to RPS.
- ③ Apply the voltage (say 5V) and note the ammeter readings.
- ④ Gradually increase the supply of voltage in steps.
- ⑤ Note the readings of ammeter.
- ⑥ Sum up the ammeter readings ( $I_1$  and  $I_2$ ), that should be equal to total current ( $I$ ).
- ⑦ Thus KCL is verified practically.



Observations:- For KVL:

Applied voltage (volts)	V <sub>1</sub> (volts)		V <sub>2</sub> (volts)		V <sub>3</sub> (volts)		V <sub>1</sub> +V <sub>2</sub> +V <sub>3</sub> (volts)	
	Theoretical	practical	Theoretical	practical	Theoretical	practical	Theoretical	practical
6V	0.45V	0.47V	0.99V	1.02V	4.54V	4.62V	5.98V	6.11V

## FOR KCL:

Applied voltage (volts)	I <sub>1</sub> (A)		I <sub>2</sub> (A)		I <sub>3</sub> (A)		I <sub>1</sub> +I <sub>2</sub> +I <sub>3</sub> (A)	
	Theoretical	practical	Theoretical	practical	Theoretical	practical	Theoretical	practical
6V	60mA	60.9mA	27.2mA	27.5mA	6mA	6.1mA	93.2mA	94.5mA

Precautions: ① Check for proper connections before switching ON the Supply.

② Make sure of proper colour coding of resistors.

③ The terminal of the resistance should be properly connected.

Calculations:- Theoretical calculations:-

FOR KVL:

$$R_{eq} = R_1 + R_2 + R_3$$

$$= 100 + 220 + 1000$$

$$= 1320 \Omega$$

$$I = V_3 / R = 6 / 1320 = 0.0045$$

$$V_1 = I R_1 = 0.0045 \times 100 = 0.45V$$

$$V_2 = I R_2 = 0.0045 \times 220 = 0.99V$$

$$V_3 = I R_3 = 0.0045 \times 1000 = 4.5V$$

$$V_1 + V_2 + V_3 = 0.43 + 0.99 + 4.54 = 5.98V$$

FOR KCL:

$$V = I R_{eq}$$

$$R_{eq} = \frac{1}{100} + \frac{1}{220} + \frac{1}{1000} = 15.5 \times 10^{-3} = 15.5 \text{ m}\Omega$$

$$I_1 = \frac{V_S}{R_1} = \frac{6}{100} = 60 \text{ mA}$$

$$I_2 = \frac{V_S}{R_2} = \frac{6}{220} = 27.2 \text{ mA}$$

$$I_3 = \frac{V_S}{R_3} = \frac{6}{1000} = 6 \text{ mA}$$

$$I_1 + I_2 + I_3 = 60 + 27.2 + 6 = 93.2 \text{ mA}$$

Result: Hence KVL and KCL are verified.

