



LABORATORY WORK SHEET

Name of the Student: MADKI SAI CHARAN

Class: CSM - 'C' Semester: Ist

Course Code: AEED03 Course Name: Electrical and Electronics Engineering Laboratory

Name of the Course Faculty: M.S.M. VARA LAKSHMI Faculty ID: IARE11072

Exercise Number: 06 Week Number: 06 Date: 03 December 2023

DAY TO DAY EVALUATION:

Marks	Aim / Preparation	Algorithm / Procedure	Source Code	Program Execution	Viva - Voce	Total
		Performance in the Lab	Calculations and Graphs	Results and Error Analysis		
Max. Marks	4	4	4	4	4	20
Obtained	4	4	4	4	4	20

Signature of Faculty

START WRITING FROM HERE :




Aim : To verify Superposition Theorem for an electrical circuit theoretically and practically.

Apparatus :

S.NO	Equipment	Range	Type	Quantity
01.	Resistor	47- Ω , 82- Ω , 100- Ω	Carbon	03.
02.	Ammeter	(0-200 mA)	Digital	01.
03.	R.P.S	(0-30V)	Digital	01.
04.	Bread Board	-	-	01.
05.	Connecting wire	-	-	As required.

Statement: In a linear, bilateral network the response in any element is equal to the sum of individual responses while all other sources are non-operative.

Circuit Diagram:

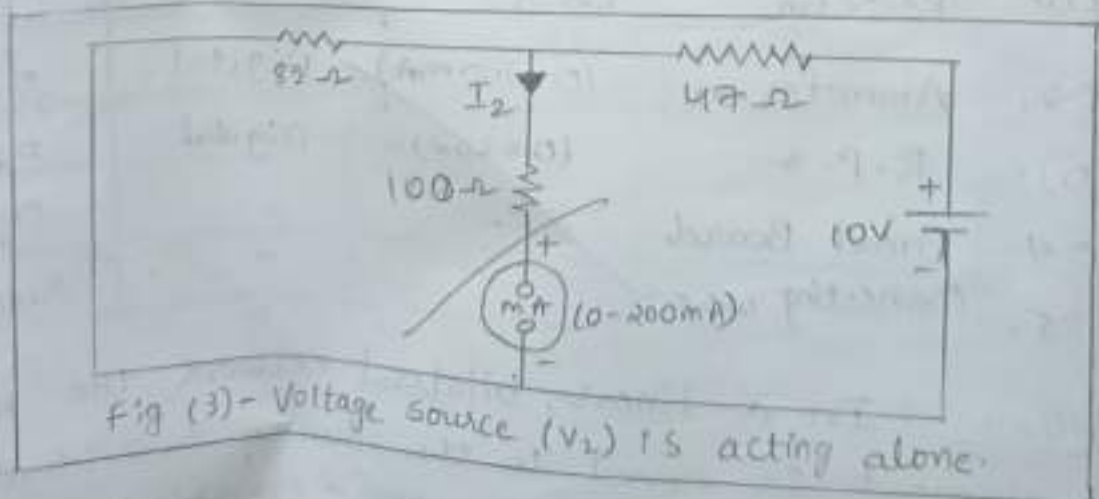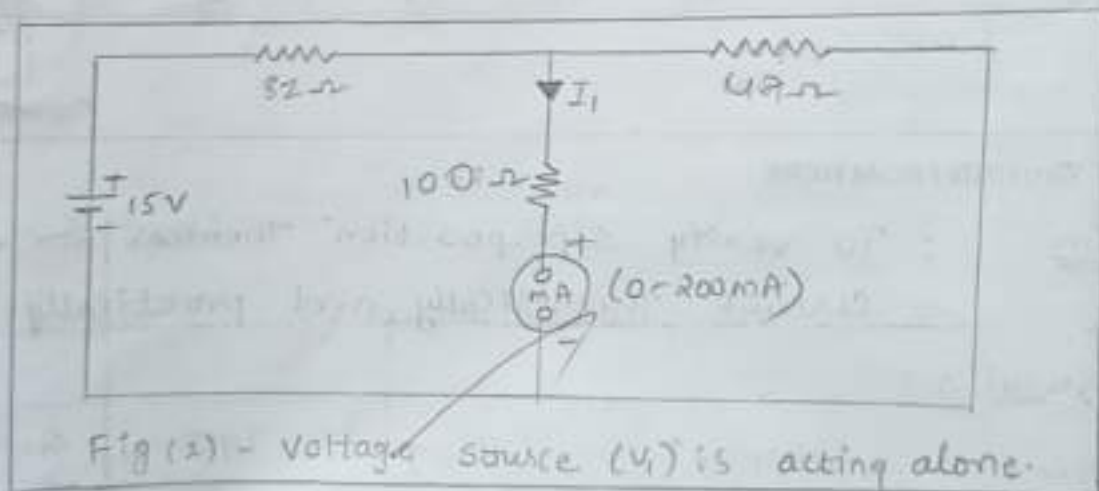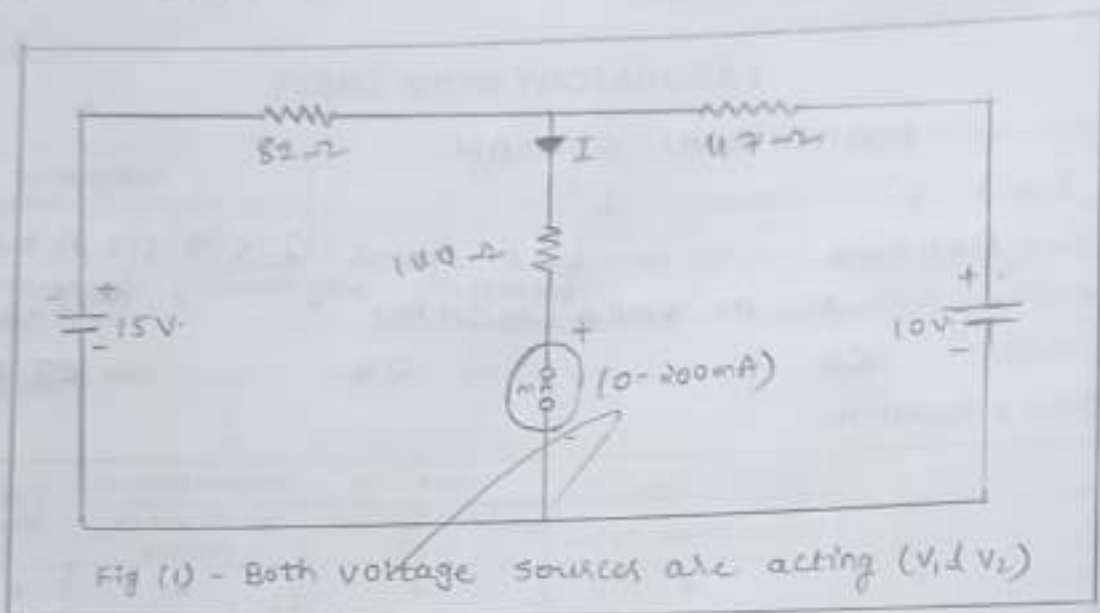

Procedure : ① Connect the circuit as shown in fig(1) and note down the current flowing through R_3 and let it be ' I '

② Connect the circuit as shown in fig(2) and note down the Ammeter Reading and let it be I_1 .


③ Connect the circuit as shown in fig(3) and note down the Ammeter Reading and let it be I_2 .

④ Verify for $I = I_1 + I_2$.

⑤ Compare the practical and theoretical currents.

Tabular column:

Parameters	When Both V_1 and $V_2 \neq 0$ (I)	When $V_1 \neq 0$ and $V_2 = 0$ (I_1)	When $V_1 = 0$ and $V_2 \neq 0$ (I_2)
Current through R_3 (Theoretical values)	90.6 mA	42.07 mA	48.6 mA
Current through R_3 (practical values)	94.5 mA	43 mA	50.7 mA

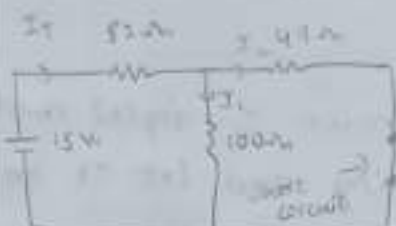Calculations:Case - 1: Making 10V energy source short circuit.

$$R_T = 82 + \left(\frac{100 \times 47}{100 + 47} \right)$$

$$R_T = 82 + 31.97$$


$$R_T = 113.97 \Omega$$

To find I_T is $I_T = \frac{V_T}{R_T} = \frac{15}{113.97} = 0.1316 A$

By current division Rule

$$I_1 = I_T \times \frac{47}{100 + 47} = 0.1316 \times 0.3197 = 0.04207$$

$$I_1 = 42.07 \text{ mA}$$

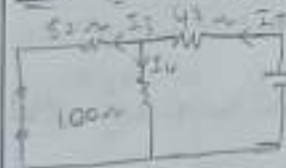Case - 2: Making 15V energy source short circuit.

$$R_T = 47 + \left(\frac{82 \times 100}{82 + 100} \right) = 47 + 45.05$$

$$R_T = 92.05 \Omega$$

To find I_T ; $I_T = \frac{V_T}{R_T} = \frac{10}{92.05} = 0.1086 A$

By current division rule.

$$I_4 = I_T \times \frac{82}{82 + 100} = 0.1086 \times \frac{82}{182} = 0.0496 A$$

$$I_4 = 49.6 \text{ mA}$$

Case - 3: Finding I ,

$$I = I_1 + I_4 = 42.07 + 49.6$$

$$I = 90.67 \text{ mA}$$



LABORATORY WORK SHEET

Name of the Student _____

Class _____

Semester _____

Course Code _____

Course Name _____

Name of the Course Faculty _____

Faculty ID _____

Exercise Number _____

Week Number _____


Date _____

DAY TO DAY EVALUATION:

Marks	Aim / Preparation	Algorithm / Procedure	Source Code	Program Execution	Viva - Voce	Total
		Performance in the Lab	Calculations and Graphs	Results and Error Analysis		
Max. Marks	4	4	4	4	4	20
Obtained						

Signature of Faculty _____

START WRITING FROM HERE :

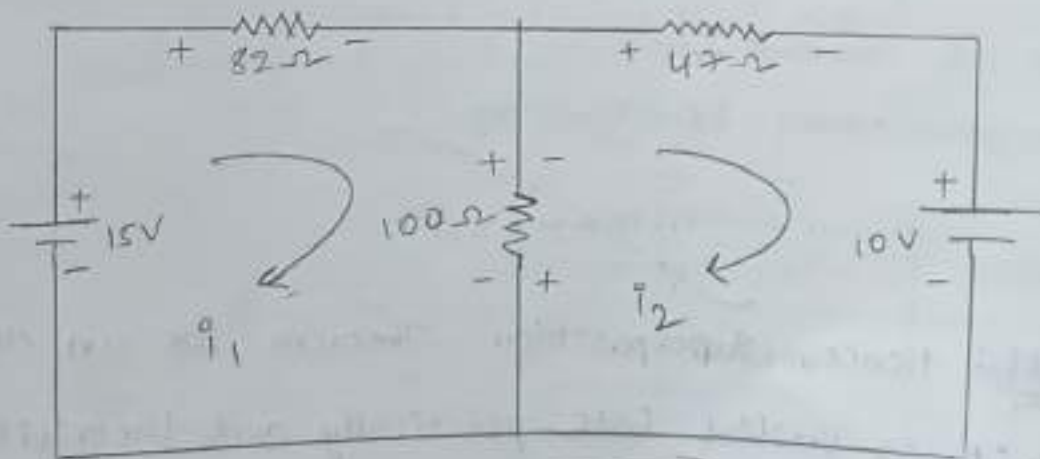

Applying KVL: $15 - 82I_1 - 100(I_1 - I_2) = 0$

$$15 - 82I_1 - 100I_1 + 100I_2 = 0$$

$$-182I_1 + 100I_2 + 15 = 0$$

$$182I_1 - 100I_2 - 15 = 0 \quad \text{--- (1)}$$

$$-47i_2 - 10 - 100(i_2 - i_1) = 0$$

$$-47i_2 - 100i_2 + 100i_1 - 10 = 0$$

$$100i_1 - 147i_2 - 10 = 0 \quad (2)$$

$$i_{100\Omega} = i_1 - i_2 \quad (3)$$

Solving (1) & (2)

$$i_1 = 0.07193$$

$$i_2 = -0.01909$$

from (3) $i_{100} = i_1 - i_2$

$$i_{100\Omega} = 0.07193 - (-0.01909)$$

$$i_{100\Omega} = 0.07193 + 0.01909$$

$$i_{100\Omega} = 0.09102 \text{ A}$$

$$i_{100\Omega} = 91.0 \text{ mA}$$

Result: Hence, superposition theorem for an electrical circuit is verified both practically and theoretically.

