


**IARE****INSTITUTE OF
AERONAUTICAL ENGINEERING**(An Autonomous Institute affiliated to JNTU, Hyderabad)
Dundigal, Hyderabad - 500 043**LABORATORY WORK SHEET**Name of the Student: MADKI SAI CHARANClass: CSM-'C'Semester: IST

Roll Number

2	3	9	5	1	A	6	6	F	2
---	---	---	---	---	---	---	---	---	---

Course Code: AMED02Course Name: Manufacturing
practiceName of the Course Faculty: MY. V. Mahidhar reddyFaculty ID: IARE 10333Exercise Number: 04Week Number: 04Date: 28 October 2023**DAY TO DAY EVALUATION:**

Marks	Aim / Preparation	Algorithm / Procedure	Source Code	Program Execution	Viva - Voice	Total
		Performance in the Lab	Calculations and Graphs	Results and Error Analysis		
Max. Marks	4	4	4	4	4	20
Obtained	4	4	4	4	4	20

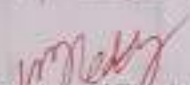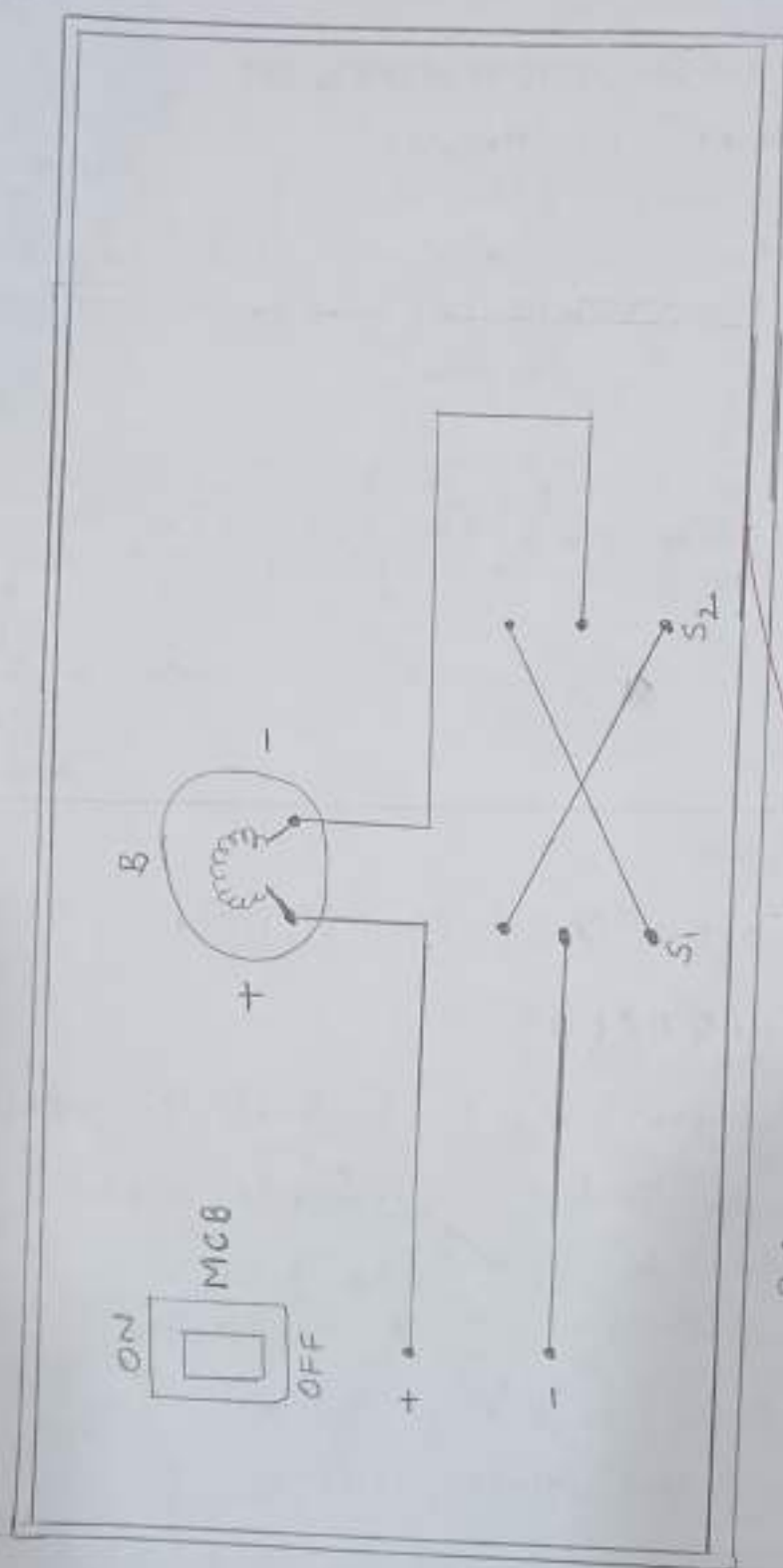

Signature of Faculty**START WRITING FROM HERE :**AIM : STAIR CASE CONNECTION.MATERIAL REQUIRED:

- | | |
|---|------------------|
| 1. Panel board | 6. Bulb 40 watts |
| 2. Mini circuit breaker | 7. Bulb holders |
| 3. Insulation tape | 8. Screws |
| 4. Wire connections | 9. Switches |
| 5. Colour code wires 1mm square
Red, Yellow, Blue, Black, Green. | |

Tools required:

- | | | |
|-------------------------|---------------------|----------------|
| 1. Tester. | 3. screw driver. | 5. wire gauge. |
| 2. cutting plier. | 4. Nose plier. | 6. pocker. |
| 7. Diagonal wire cutter | 8. Ball pen hammer. | |

Diagram:



240 Volts

B = Bulb

S = Switch

Sequence of operations:

1. Off the MCB.
2. Measuring the wires (1mm sq.)
3. Wire sleeving
4. Wire connecting.
5. Finishing.

Procedure:

① Take two switches and 2 1mm sq. wires of Red.

② Remove the surface layer of wire with help of diagonal wire cutter and straighten the thin wires with help of nose plier.

③ In switches remove the screws with help of screw driver and join the wires and to each other switches & set back the screw with help of screw driver.

④ Take another 1mm red & Black wire and connect it to 40 Watt Bulbs and it shall be on bulb holder.

⑤ Make sure that the another red wire which is connected to ^{either} any one of the switches and and black wire which is connected to bulb shall be connected to MCB and then to panel board and switch on the MCB.

Safety precautions:

- ① Wear apron, wear shoes.
- ② Make sure to wear gloves.
- ③ make sure there is a sufficient enough power supply.
- ④ Use the Insulation tapes necessary wherever at wire breakage connections.

Result:- we observe that when we on one switch and off one switch, the bulb doesnot glows. Besides, If we on the 2 switches, the connection is there and hence the bulb glows.