

## LABORATORY WORK SHEET

Name of the Student : Abdul Basith Khan  
 Class (C.S.M.-A) 1<sup>st</sup> Year Semester 1<sup>st</sup>  
 Course Code : AEED001 Course Name : EEE Laboratory  
 Name of the Course Faculty : Dr. L. Rajashekhar Goud Faculty ID : IARE11067  
 Exercise Number : 04 Week Number : 04 Date :

Roll Number									
2	3	9	5	1	A	6	6	0	1

### DAY TO DAY EVALUATION:

Marks	Aim / Preparation	Algorithm / Procedure	Source Code	Program Execution	Viva Voce	Total
		Performance in the Lab	Calculations and Graphs	Results and Error Analysis		
Max. Marks	4	4	4	4	4	20
Obtained	4	4	4	4	4	19

Signature of Faculty

### START WRITING FROM HERE :


### Nodal Analysis :-

#### Aim:-

The study of nodal analysis is the objectives of this exercise specifically its usage in multi-source DC circuits. Its application in finding circuit node voltage will be investigated.

#### Apparatus:-

S. No.	Equipment	Range at	Type	Quantity
1.	Resistor	1k $\Omega$ , 470 $\Omega$ , 220 $\Omega$ , 150 $\Omega$ , 100 $\Omega$	Carbon	6
2.	Voltmeter	0-20V	Digital	01
3.	RPS	0-30V	Digital	01
4.	Breadboard	-	-	01
5.	Connecting wires	-	-	As required

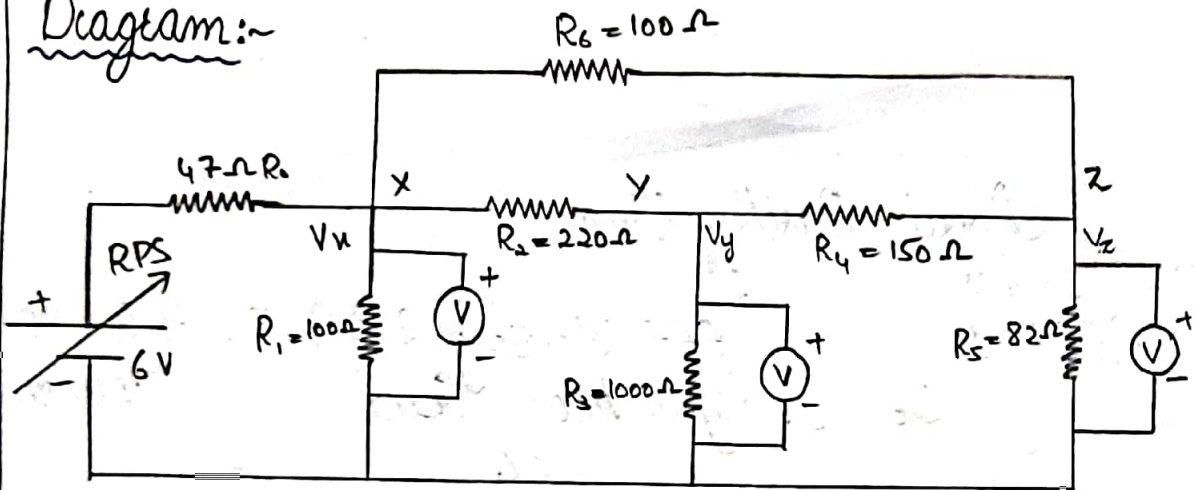Diagram:-Observation:-

Applied Voltage $V$ (volts)	Node Voltage $V_1$ (volts)		Node Voltage ( $V_2$ ) (volts)		Node Voltage ( $V_3$ ) (volts)	
	Theoretical	Practical	Theoretical	Practical	Theoretical	Practical
6V	3.7	3.6	2.5	2.4	1.7	1.5

Procedure:-

1. Connect the circuit diagram as shown in figure.
2. Switch on the supply to RPS.
3. Apply the voltage (say 15V) and note the voltmeter readings.
4. Gradually increases the supply voltage in steps.
5. Note the readings of voltmeter.
6. Verify the practical results obtained with theoretical results.

Precautions:-

- To check for proper connections before switching on the power supply.
- Make sure of proper colour coding of resistors.
- The terminal of the resistance should be properly connected.

### Calculations:-

Apply KCL at node 'u':

$$I_1 + I_2 + I_3 + I_4 = 0$$

$$\frac{V_x - 6}{47} + \frac{V_x - 0}{100} + \frac{V_x - V_y}{220} + \frac{V_x - V_z}{100} = 0$$

$$V_x \left[ \frac{1}{47} + \frac{1}{100} + \frac{1}{220} + \frac{1}{100} \right] - \frac{6}{47} - \frac{V_y}{220} - \frac{V_z}{100} = 0$$

$$V_x (0.04) - 0.12 - 0.004 V_y - 0.01 V_z = 0$$

$$0.04 V_x - 0.004 V_y - 0.01 V_z = 0.12 \quad \text{--- (1)}$$

Apply KCL at node 'y':

$$I_3 + I_5 + I_6 = 0$$

$$\frac{V_y - V_x}{220} + \frac{V_y - V_z}{150} + \frac{V_y - 0}{1000} = 0$$

$$V_y \left[ \frac{1}{220} + \frac{1}{150} + \frac{1}{1000} \right] - \frac{V_x}{220} - \frac{V_z}{150} = 0$$

$$0.01 V_y - 0.004 V_x - 0.006 V_z = 0$$

$$-0.004 V_x + 0.01 V_y - 0.006 V_z = 0 \quad \text{--- (2)}$$

Apply KCL at node 'z':

$$I_5 + I_4 + I_7 = 0$$

$$\frac{V_z - V_y}{150} + \frac{V_z - V_x}{100} + \frac{V_z - 0}{82} = 0$$

$$V_z \left[ \frac{1}{150} + \frac{1}{100} + \frac{1}{82} \right] - \frac{V_y}{150} - \frac{V_x}{100} = 0$$

$$0.03 V_z - 0.06 V_y - 0.01 V_x = 0$$

$$-0.01 V_x - 0.06 V_y + 0.03 V_z = 0 \quad \text{--- (3)}$$

By solving equations (1), (2) & (3)



$$V_x = 3.7V$$

$$V_y = 2.5V$$

$$V_z = 1.7V$$

Result:-

Hence nodal analysis is verified both theoretically and practically