

**IARE****INSTITUTE OF  
AERONAUTICAL ENGINEERING**(An Autonomous Institute affiliated to JNTU(H, Hyderabad)  
Dundigal, Hyderabad - 500 043**LABORATORY WORK SHEET**Name of the Student : MA D KI SAI CHARANClass : CSM - 'C'Semester : I<sup>st</sup>

Roll Number

23951AG6F2Course Code : AEE003Course Name : Electrical and  
Electronics Engineering LaboratoryName of the Course Faculty : MS. M. VARA LAKSHMIFaculty ID : IARE 11072Exercise Number : 07Week Number : 07Date : 22 December 2023**DAY TO DAY EVALUATION:**

Marks	Aim / Preparation	Algorithm / Procedure	Source Code	Program Execution	Viva - Voce	Total
		Performance in the Lab	Calculations and Graphs	Results and Error Analysis		
Max. Marks	4	4	4	4	4	20
Obtained	4	4	4	4	4	20

Signature of Faculty

**START WRITING FROM HERE :**




Aim : TO Verify the Condition of reciprocity for an electric network theoretically and practically.

Apparatus :

S.NO	Name of the Equipment	Range	Type	Quantity
01.	Ammeter	[0-200mA]	Digital	01
02.	Voltmeter	[0-30V]	Digital	01
03.	R.P.S	[0-30V]	Digital	01
04.	Resistors	100Ω, 150Ω, 10k, 220k, 47k	-	05
05.	Bread Board	-	-	01
06.	Connecting wires	-	-	As required.

Statement : In any linear, bilateral, single source network the ratio of excitation to response is constant even when their positions are inter changed.

Circuit Diagram:

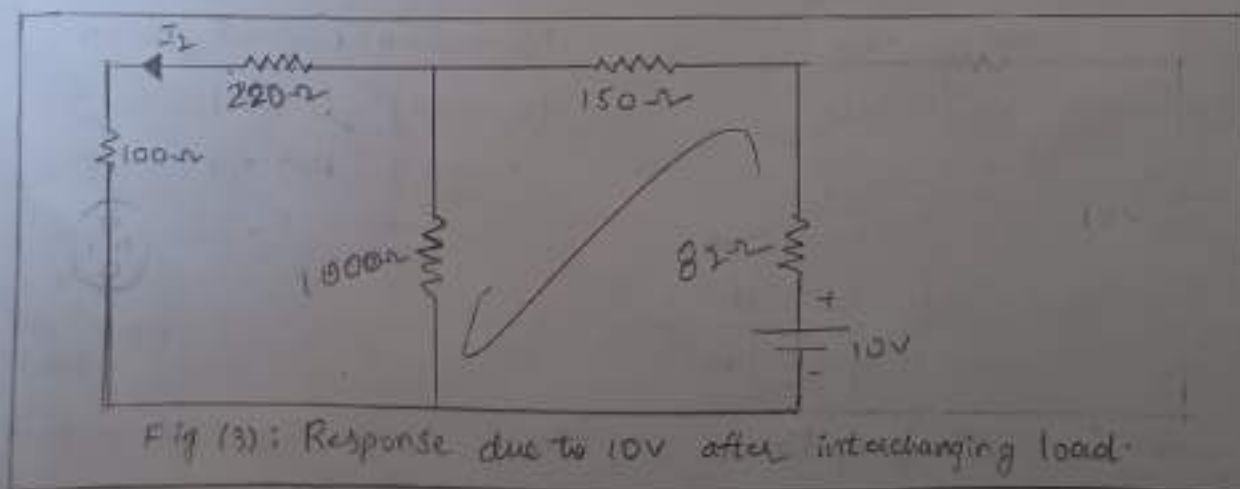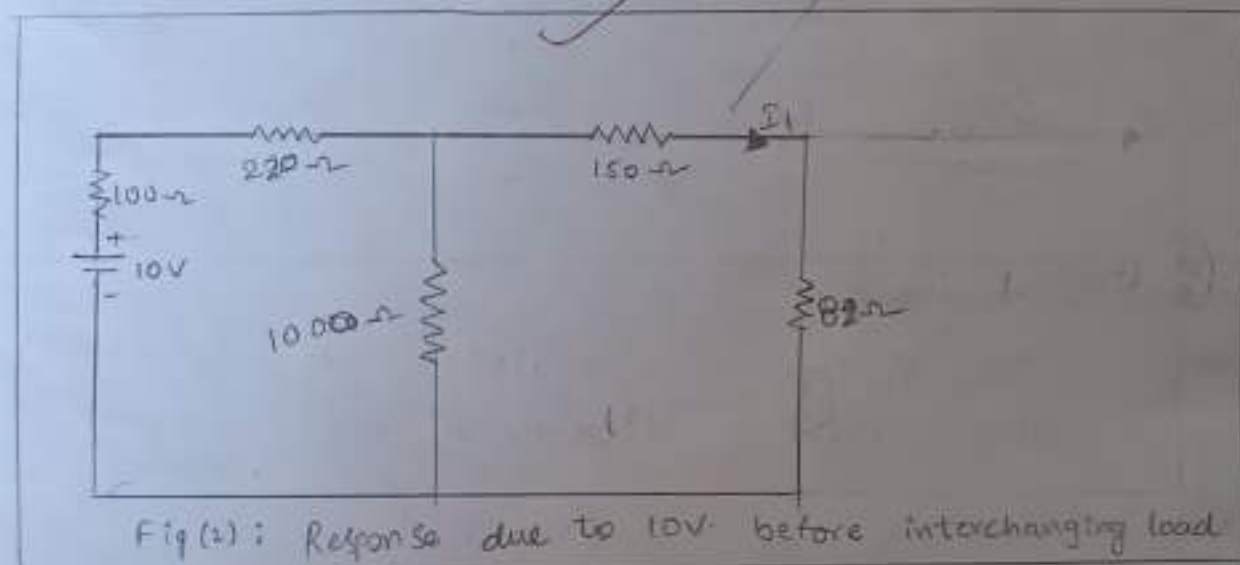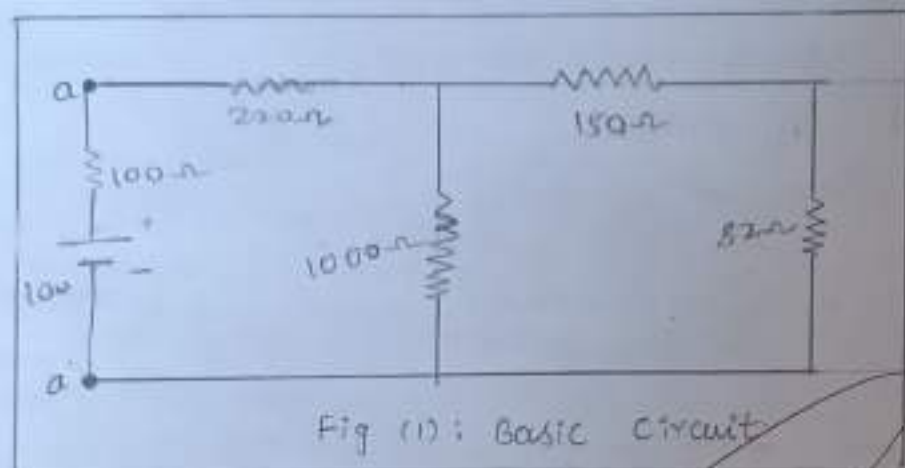

- Procedure:
- ① Connect the circuit as shown in fig (2).
  - ② Measure the current  $I_1$  in the branch.
  - ③ Inter-change voltage source and response as shown in fig (3) and note down the current  $I_2$ .
  - ④ Observe that the currents  $I_1$  and  $I_2$  should be same.
  - ⑤ Measure the ratio of excitation and response and check whether they are equal in both cases.

### Calculations:

From fig (2)

$$R_{eq} = \left( \frac{232 \times 1000}{1232} \right) + 220 + 100 = 508.13 \Omega$$

$$I_T = \frac{10}{508.31} = 0.019 A = 19 \times 10^{-3} A$$

$$I_T = 19 mA$$

$$I_1 = \frac{OPD}{Total} \times I_T$$

$$I_1 = 0.019 \times \frac{1000}{1232} \Rightarrow I_1 = 0.0154 A$$

$$V/I_1 = 649.35$$

From fig (3)

$$R_{eq} = \left( \frac{320 \times 100}{1320} \right) + 150 + 82$$

$$R_{eq} = 474.42 \Omega$$



$$I_T = \frac{10}{474.42} = 0.021 \text{ A}$$

$$I_T = 21 \text{ mA}$$

$$I_2 = I_T \times \frac{R_{PP}}{R_{Total}} = 0.021 \times \frac{1000}{1320}$$

$$I_2 = 0.0159 \text{ A}$$

$$V/I_2 = 649.35$$

$$\Rightarrow V/I_1 = V/I_2$$

Tabular column:

Parameters	Theoretical values	practical values
$I_1$	15.4 mA	16.4 mA
$I_2$	15.4 mA	16.1 mA

Precautions:

- ① check for proper connections before switching ON the supply.
- ② Make sure of proper colour coding of resistors.
- ③ The terminal of the resistance should be properly connected.

Result:

Hence, Reciprocity theorem for an electric circuit network is verified both theoretically and practically.

