



# INSTITUTE OF AERONAUTICAL ENGINEERING

(Autonomous)

Dundigal, Hyderabad - 500 043

B.TECH I SEMESTER CIE – I EXAMINATIONS, NOVEMBER – 2023

Regulation: BT23

ELEMENTS OF ELECTRICAL AND ELECTRONICS ENGINEERING  
(COMMON TO AE | CSE(AI&ML) | IT | ME | CE)

Time: 2 Hours

Max Marks: 20

Answer any FOUR questions

All parts of the question must be answered in one place only

1. (a) Summarize the following terms

- |                    |                        |
|--------------------|------------------------|
| i) Peak value      | ii) Peak to peak value |
| iii) Average value | iv) RMS value          |
| v) Peak factor     | vi) Form factor        |

[BL: Understand| CO: 1|Marks: 2]

- (b) Apply mesh analysis for Figure 1 and calculate the current through
- $8\Omega$
- resistance.

[BL: Apply| CO: 1|Marks: 3]

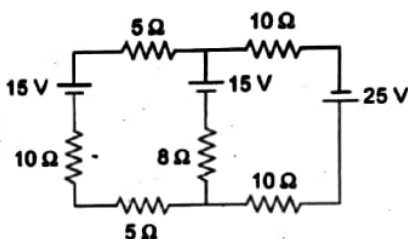


Figure 1

2. (a) State and explain Kirchhoff's voltage law and Kirchhoff's current law with neat diagram.

[BL: Understand| CO: 1|Marks: 2]

- (b) A sinusoidal voltage applied to an inductor
- $2\text{mH}$
- . The frequency of sine wave is
- $3\text{KHz}$
- . Determine the inductive reactance.

[BL: Apply| CO: 1|Marks: 3]

3. (a) State and verify maximum power transfer theorem with an example for DC excitation.

[BL: Understand| CO: 2|Marks: 2]

- (b) Determine the current flowing through
- $3\text{ ohms}$
- resistor using Thevenin's theorem for the circuit shown in Figure 2.

[BL: Apply| CO: 2|Marks: 3]

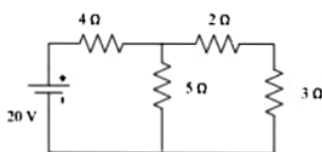


Figure 2

4. (a) Derive the relationship between line and phase voltage in a 3-phase unbalanced delta connected system.

[BL: Understand| CO: 2|Marks: 2]

- (b) Three impedance each
- $5 + j12\Omega$
- is connected in star are connected to a
- $220\text{ V}$
- three phase,
- $50\text{Hz}$
- supply. Calculate the line currents and the power drawn by the circuit.

[BL: Apply| CO: 2|Marks: 3]

5. (a) State the principle of DC generator. Explain the working of DC generators with neat diagram.

[BL: Understand| CO: 3|Marks: 2]

- (b) A 4 pole DC generator having wave wound armature has 50 slots and 25 conductors per slot. Find the generated emf, if it is driven at
- $25\text{RPM}$
- and useful flux per pole in the machine is
- $0.03\text{ Wb}$
- .

[BL: Apply| CO: 3|Marks: 3]