



**IARE**  
INSTITUTE OF  
AERONAUTICAL ENGINEERING  
(An Autonomous Institute affiliated to JNTU, Hyderabad)  
Dundigal, Hyderabad - 500 043

## LABORATORY WORK SHEET

Name of the Student : Abdul Basith Khan

Class : 1<sup>st</sup> Year (CSEM-A) Semester : 1<sup>st</sup>

Course Code : AEE001 Course Name : EEE Laboratory

Name of the Course Faculty : Dr. Rajashekhara Goud Faculty ID : IARE/11067

Exercise Number : 05 Week Number : 05 Date : \_\_\_\_\_

Roll Number									
2	3	9	5	1	A	6	6	0	1

### DAY TO DAY EVALUATION:

Marks	Aim / Preparation	Algorithm / Procedure	Source Code	Program Execution	Viva - Voce	Total
		Performance in the Lab	Calculations and Graphs	Results and Error Analysis		
Max. Marks	4	4	4	4	4	20
Obtained	4	4	3	3	4	18

[Signature]  
Signature of Faculty

START WRITING FROM HERE :

Thevenins Theorem:-

Aim:-

To verify Thevenins Theorem for an electric current theoretically and practically.









Apparatus:-

S. No.	Equipment	Range	Type	Quantity
1.	Ammeter	0-200mA	Digital	1
2.	Voltmeter	0-30V	Digital	1
3.	RPS	0-30V	Digital	1
4.	Bread Board	-	-	1
5.	Resistors	82 $\Omega$ , 150 $\Omega$ 47 $\Omega$ , 100 $\Omega$	-	4
6.	Connecting wires	- 1/4	-	As required

## Theory:-

Any bilateral linear active network can be replaced by a Thevenins equivalent voltage source ' $V_{th}$ ' in series with a Thevenins equivalent resistance ' $R_{th}$ '.

## Circuit Diagram:-

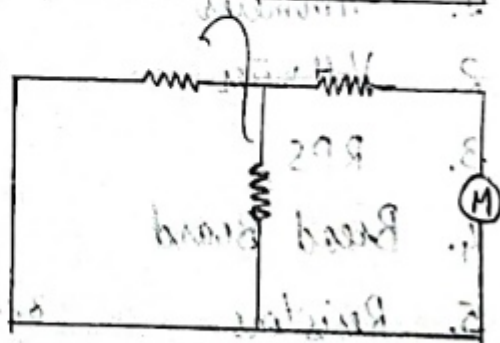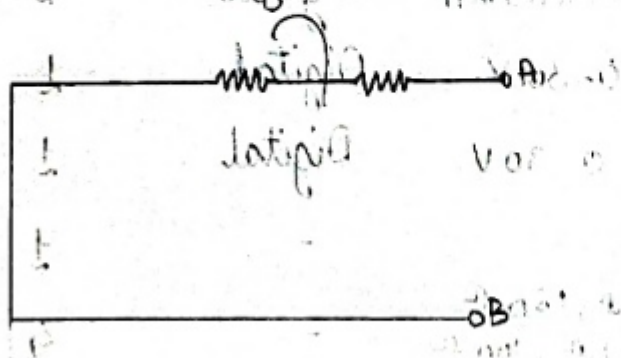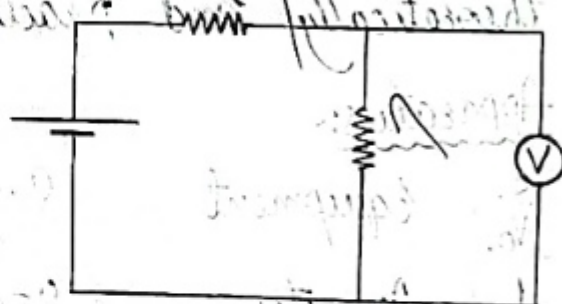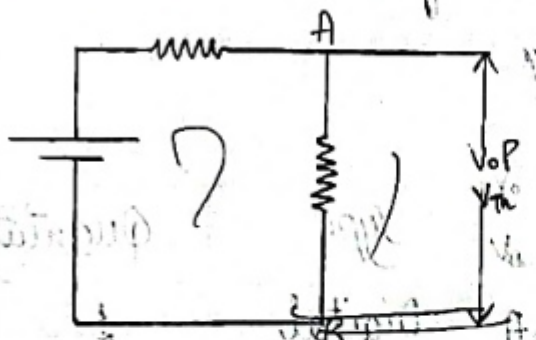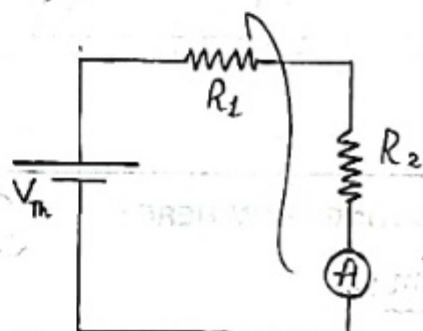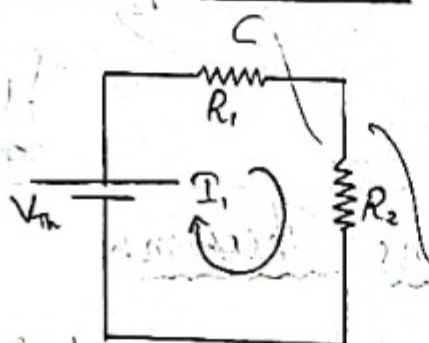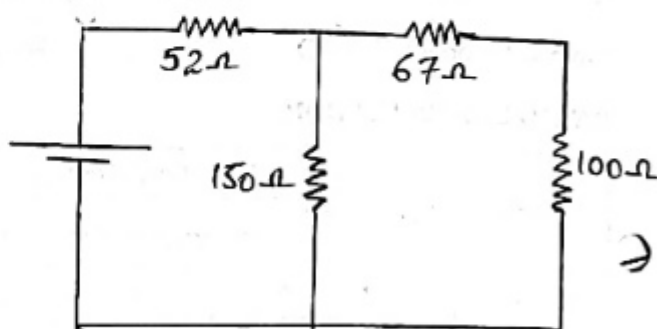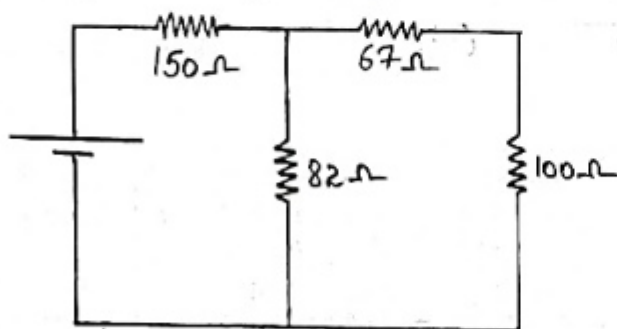

Observations:-

Parameters	Theoretical	Practical
$V_o$	9.64 V	9.64 V
$R_{Th}$	100.01 $\Omega$	101.9 $\Omega$
$I_2$	0.45 A	0.046 A

Series with a Thevenins equivalent  $R_{Th}$ .

Procedure:-

1. Connect the circuit diagram as shown in the fig.
2. Measure current in  $R_2$ .
3. Connect circuit as shown in a figure - measure open circuit voltage  $V_o$  by open connecting terminal (i.e.  $V_{Th}$ ).
4. Draw the thevenins equivalent circuit.
5. Measure current in  $R_2$ .

Calculations:-

By figure from KVL

$$-15 + 82i_1 + 150i_1 = 0$$

$$232i_1 = 15$$

$$i_1 = 0.064$$

$$\text{Voltage across } 150\Omega = 150 \times i_1$$

$$= 150 \times 0.064$$

$$V_{Th} = 9.6 \text{ V}$$

$$R_{Th} = \frac{82 \times 150}{82 + 150} + 47$$



$$R_{Th} = 100.01 \Omega$$

$$\therefore I = \frac{V_{Th}}{R_{Th} + R_2}$$

We know  $R_2 = 100 \Omega$

$$I = \frac{9.6}{100.01 + 100}$$

$$I = 0.048 A$$

### Precautions:-

1. Check proper connections before supplying power.
2. Make sure of proper colour coding of resistors.
3. The terminal of the resistance should be properly connected.

### Result:-

Hence, Thevenin's theorem is verified theoretically and practically.

By figure from KVL

$$0 = 12 - 85i + 120i - 21 - 385i + 12$$

$$21 = 158i$$

$$120i = 21$$

$$120 \times 0.21 = 25.2 \text{ mV}$$

$$120 \times 0.21 =$$

$$V_{Th} = 25.2 \text{ mV}$$

$$I = \frac{0.21 \times 25.2}{0.21 + 38}$$