

## LABORATORY WORK SHEET

Name of the Student : Abdul Basith Khan  
 Class : 1<sup>st</sup> Year (CSM-A) Semester : 1<sup>st</sup>  
 Course Code : AECDO1 Course Name : EEE Laboratory  
 Name of the Course Faculty : Dr. L. Rajashekhara Goud Faculty ID : IARE11067  
 Exercise Number : 11 Week Number : 11 Date : 21/01/2024

Roll Number									
2	3	9	5	1	A	6	6	0	1

### DAY TO DAY EVALUATION:

Marks	Aim / Preparation	Algorithm / Procedure	Source Code	Program Execution	Viva - Voce	Total
		Performance in the Lab	Calculations and Graphs	Results and Error Analysis		
Max. Marks	4	4	4	4	4	20
Obtained	4	4	4	3	4	19

Signature of Faculty

### START WRITING FROM HERE :

Zener Diode as Voltage Regulator:-

$$V_{in} = 15V$$

$$V_{NL} =$$

$R_L (\Omega)$	$V_{FL}$ (Volts)	$I_L$ (mA)	% Regulation
100	1.56	14.2	0.67
200	2.73	13	0.43
500	4.43	8.8	0.07
1K	4.67	4.7	0.02
2K	4.73	2.4	0.01
5K	4.77	1.0	0.5
10K	4.78	0.5	0.75
20K	4.78	0.2	0.90

$R_L = 15k$ 

$E_s$ (Volts)	$E_{FL}$ (Volts)	$I_L$ (mA)
1	1.10	0.1
2	1.97	0.1
4	3.62	0.2
6	4.31	0.3
8	4.53	0.3
10	4.64	0.3
12	4.71	0.3
14	4.76	0.3

### Precautions:-

1. Ensure that the polarities of the power supply and the meters as per the circuit diagram.
2. Keep the input voltage knob of the regulated power supply in minimum position both when switching ON or Switching OFF.
3. OFF the power supply.
4. No loose contacts at the junction.
5. Ensure that the ratings of the meters as per the circuit diagram for precision.

### Calculations:-

Forward static resistance at 6mA =  $\frac{E_F}{I_F}$

Forward Dynamic resistance at 6mA =  $\frac{\Delta E_f}{\Delta I_f}$

Reverse static resistance at 6mA =  $\frac{E_F}{I_F}$

Reverse Dynamic resistance at  $6\text{mA} = \Delta E_f / \Delta I_f$

Result:-

1. V-I characteristics of zener diode are plotted and verified in both forward and backward directions.

2. Zener breakdown voltage for  $4.7\text{V}$

Zener Diode =  $4.7\text{V}$

3. (i) Reverse Bias:-

a) Static resistance at  $6\text{mA}$

b) Dynamic resistance at  $6\text{mA}$

(ii) Forward Bias:-

a) Static resistance at  $6\text{mA}$

b) Dynamic resistance at  $6\text{mA}$