

## LABORATORY WORK SHEET

Name of the Student : Abdul Basith Khan  
 Class : 1<sup>st</sup> Year (CSM-A) Semester : I<sup>st</sup>  
 Course Code : AEEED01 Course Name : EEE laboratory  
 Name of the Course Faculty : Dr. L Rajashekhara Goud Faculty ID : IARE11067  
 Exercise Number : 07 Week Number : 07 Date : 13/01/2024

### DAY TO DAY EVALUATION:

Marks	Aim / Preparation	Algorithm / Procedure	Source Code	Program Execution	Viva - Voce	Total
		Performance in the Lab	Calculations and Graphs	Results and Error Analysis		
Max. Marks	4	4	4	4	4	20
Obtained	4	4	4	4	4	20

Signature of Faculty

### START WRITING FROM HERE :

Reciprocity Theorem:-

AIM:-

To verify and the combination of reciprocity for electric network theoretically and practically.




Apparatus:-

S.No	Name of the equipment	Range	Type	Quantity
1.	Ammeter	(0-200)mA	Digital	01
2.	Voltmeter	(0-30) V	Digital	01
3.	RPS	(0-30) V	Digital	01
4.	Resistors	100 $\Omega$ , 150 $\Omega$ 1K $\Omega$ , 220 $\Omega$ , 82 $\Omega$	-	05
5.	Bread Board	-	-	01
6.	Connecting Wires	1/4	-	As Required

Statement:-

In any linear bilateral signal i.e. source at work the ratio of excitation to response is constant even there positive

Circuit Diagram:-

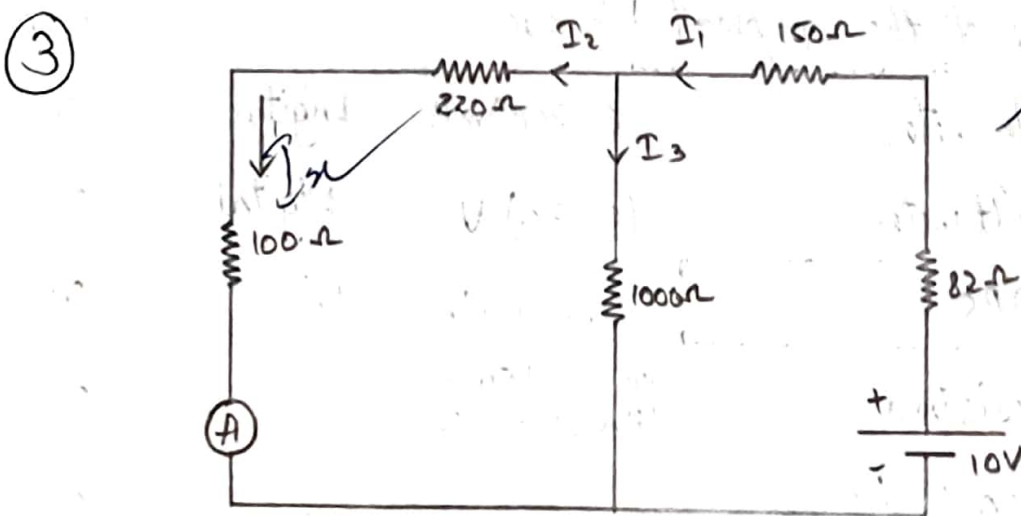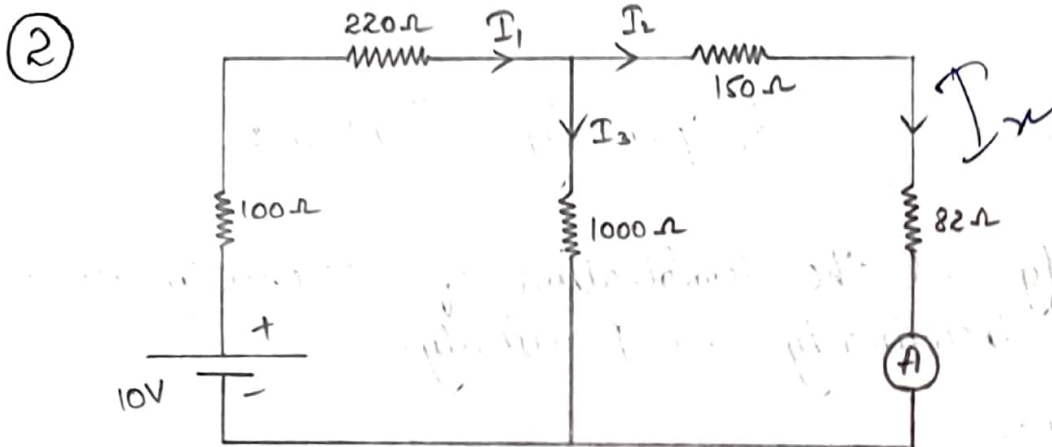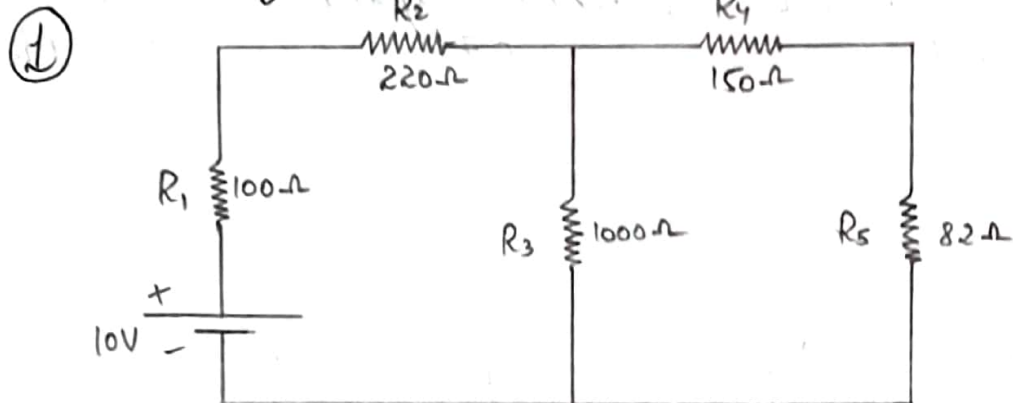

Procedure:-

- 1) Connect the circuit as shown in fig (1)
- 2) Measure the current  $I_1$  in the branch
- 3) Later change voltage source and response as shown in fig (2) and note down the current  $I_2$ .
- 4) Observe that the currents  $I_1$  and  $I_2$  should be same.
- 5) Measure the ratio of excitation and response and check whether they are equal in both cases.

Calculations:-Theoretical Calculations:-Case (i):-

$$\begin{aligned}
 R_{eq} &= \frac{232 \times 1000}{1000 + 23} + 220 + 100 \\
 &= \frac{232000}{1232} + 320 \\
 &= 188.311 + 320
 \end{aligned}$$

$$R_{eq} = 508.311 \Omega$$

$$I_1 = \frac{10}{508.311}$$

$$I_1 = 0.018 A$$

$$I_2 = 0.018 \times \frac{1000}{1232}$$

$$= 0.018 \times 0.811$$

$$I_2 = 0.015 A$$

$$I_3 = I_2 - I_1$$

$$= 0.018 - 0.015$$

$$I_3 = 0.003 A$$



Case (ii):  $R_{eq} = \frac{320 \times 1000}{1320} + 82 + 150$   
 $= \frac{320000}{1320} + 232$

$$R_{eq} = 474.424 \Omega$$

$$I_1 = \frac{10}{474.42} \Rightarrow I_1 = 0.021 A$$

$$I_2 = 0.021 \times \frac{1000}{1320} \Rightarrow I_2 = 0.015 A$$

$$I_3 = 0.021 - 0.015 \Rightarrow I_3 = 0.006 A$$

Tabular Column:

Parameter	Theoretical Values	Practical Values
Case (i)	0.018 A	0.019 A
Case (ii)	0.015 A	0.019 A

Precautions:

Check for proper connections before switching on the supply make sure of proper colour coding of resistor the terminal of the resistance should be properly connected.

Result:

Hence the Reciprocity theorem is an electric circuit network verified both theoretically and practically.