



### LABORATORY WORK SHEET

Name of the Student: MADKI SAI CHARAN

Class: C.S.M. - 'C' Semester: I<sup>st</sup>

Course Code: AEEED03 Course Name: Electrical and

Name of the Course Faculty: M.S.M. VARALAKSHMI

Exercise Number: 05 Week Number: 05

Date: 01 December 2023

Roll Number									
2	3	9	5	1	A	6	6	F	2

Faculty ID: IARE 11072

#### DAY TO DAY EVALUATION:

Marks	Aim / Preparation	Algorithm / Procedure	Source Code	Program Execution	Viva - Voce	Total
		Performance in the Lab	Calculations and Graphs	Results and Error Analysis		
Max. Marks	4	4	4	4	4	20
Obtained	4	4	4	4	4	20

Signature of Faculty

#### START WRITING FROM HERE :



Aim : To verify Norton's theorem for electrical circuit theoretically and practically.


#### Apparatus :

S.No	Equipment	Range	Type	Quantity
01.	Ammeter	(0-200mA)	Digital	01
02.	Voltmeter	(0-20V)	Digital	01
03.	R.P.S	(0-30V)	Digital	01
04.	Bread Board	-	-	01
05.	Resistors	82 $\Omega$ , 47 $\Omega$ , 100 $\Omega$ , 150 $\Omega$	-	04
06.	Connecting wires	-	-	As required

Statement: Any linear, Bilateral network with current sources, voltage sources and resistances can be replaced by an equivalent circuit consisting of a current source in parallel with a resistance. The value of the current source is the current flowing through the short circuit terminals of the network and the resistance is the equivalent resistance measured between the open circuit terminals of the network with all the energy sources replaced by the internal resistance.

Circuit Diagram:

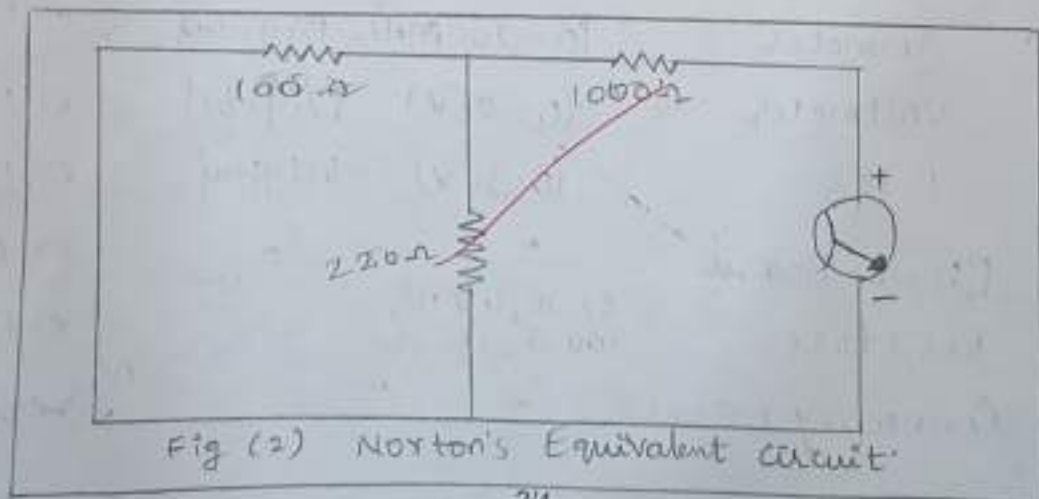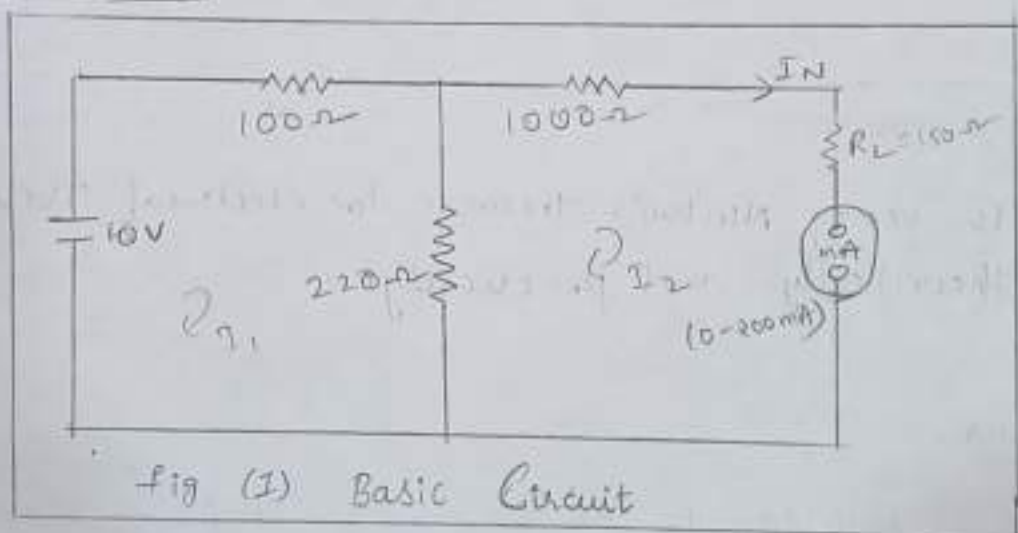

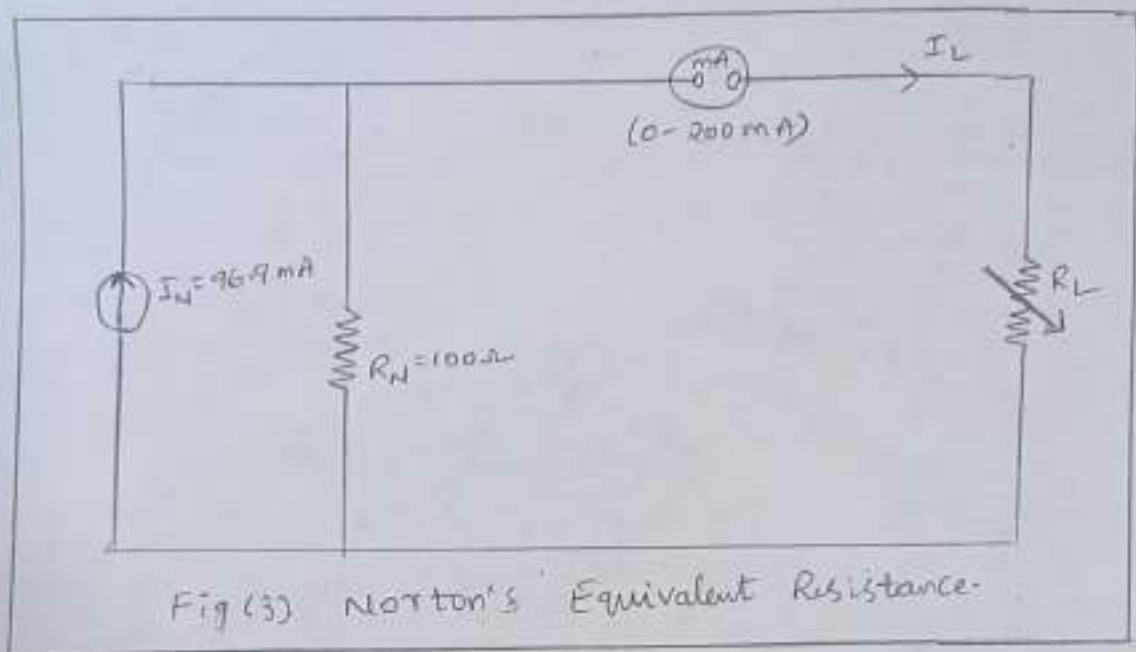

Procedure :- ① Connect the circuit diagram as shown in fig (1).

② Measure the current  $I_{sc}$  (or)  $I_N$  through short circuited terminal.

③ Connect the circuit diagram as shown in fig (2).

④ Find the resistance between open circuited terminals by using multimeter.

⑤ Draw Norton's equivalent circuit by connecting  $I_N$  &  $R_N$  in parallel as shown in fig (3) and find out the load current.

Tabular column :

Parameters	Theoretical values	Practical values.
$I_N$	6.43 mA	6.6 mA
$R_N$	1068.75 Ω	1051.0 Ω
$I_L$	5.64 mA	5.5 mA



Calculations:  $R_L = 150 \Omega$ 

$$R_N = \left( \frac{100 \times 220}{100 + 220} \right) + 1000 = 68.75 + 1000$$

$$R_N = 1068.75 \Omega$$

for loop-1:

$$10 - 100 I_1 - 220 (I_1 - I_2) = 0$$

$$320 I_1 - 220 I_2 = 10 \quad \text{--- (1)}$$

For loop 2:

$$1000 I_2 + 220 (I_2 - I_1) = 0$$

$$220 I_1 - 1220 I_2 = 0 \quad \text{--- (2)}$$

Solve (1) & (2); we get  $I_1 = 0.03567 \text{ A}$ 

$$I_2 = 0.00643 \text{ A}$$

$$I_N = I_2 = 0.00643 \text{ A}$$

$$I_L = I_N \times \frac{R_N}{R_N + R_L} = 0.00643 \times \frac{1068.75}{1068.75 + 150}$$

$$I_L = 0.00564 \text{ A} = 5.64 \text{ mA}$$

Result: Hence, Norton's theorem is verified both practically and Theoretically.