



LABORATORY WORK SHEET

Name of the Student : Abdul Basith Khan

Class : 1st Year (CSM-A) Semester : Ist

Course Code : AEED001 Course Name : EEE laboratory

Name of the Course Faculty : Dr. C. Rajashekhara Yous Faculty ID : IARE/11067

Exercise Number : _____ Week Number : _____ Date : _____

DAY TO DAY EVALUATION:

Marks	Aim / Preparation	Algorithm / Procedure	Source Code	Program Execution	Viva - Voce	Total
		Performance in the Lab	Calculations and Graphs	Results and Error Analysis		
Max. Marks	4	4	4	4	4	20
Obtained	4	4	4	3	4	19

Signature of Faculty

START WRITING FROM HERE :

Super position Theorem:-

Aim:-




To verify principle of super-position theorem for an electrical circuit theoretically and practically.

Apparatus:-

S.No	Equipment	Range	Type	Quantity
1.	Resistors	82 Ω , 47 Ω , 100 Ω	Carbon	03
2.	Ammeter	(0-200mA)	Digital	01
3.	R.P.S	(0-30)	Digital	01
4.	Bread Board	-	-	01
5.	Connecting			As required

Statement:-

In a linear, bilateral network the response in any element is equal to sum of individual responses while all sources are non-operative.

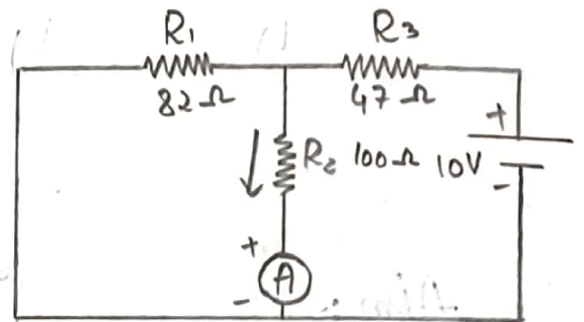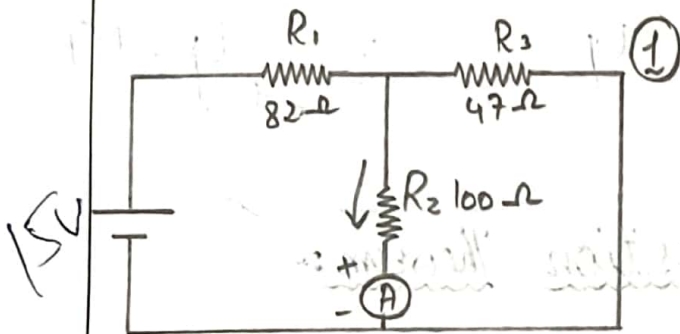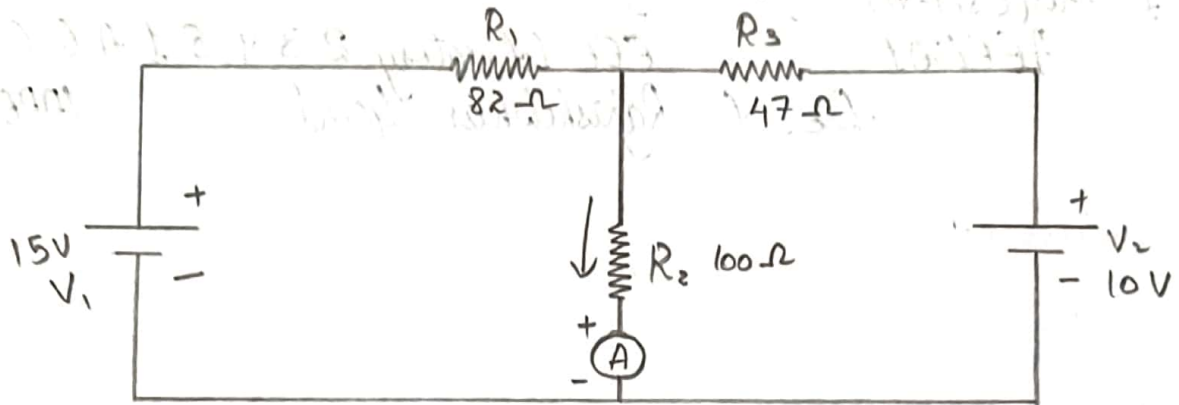Observation:-

Parameters	When both V_1 and $V_2 \neq 0$ (I)	When $V_1 \neq 0$ and $V_2 = 0$ (-)	When $V_1 = 0$ and $V_2 \neq 0$ (-)
Current through R_3 (mA) (Theoretical Values)	0.088 A	0.040 A	0.048 A
Current through R_3 (mA) (Practical Values)	0.089 A	0.042 A	0.047 A

Procedure:-

1) Convert the circuit as shown in fig(1) and note down the current flowing through R_3 and let it be I .

2) Convert the circuit as shown in figure (2) and note down the ammeter reading and let it be I_1 .

3) Connect the circuit as shown in figure (3) and note down the ammeter reading and let it be I_2 .

4) Verify for $I = I_1 + I_2$

5) Compare the practical and Theoretical current.

Calculation:-

Case (i):- $V_1 \neq 0, V_2 = 0, R_1 = 82 \Omega, R_2 = 100 \Omega, R_3 = 47 \Omega$

$$R_{eq} = R_1 + R_2 // R_3 = R_1 + \frac{R_2 R_3}{R_2 + R_3} = 82 + \frac{100 \times 47}{100 + 47}$$

$$= 82 + \frac{4700}{147} = 82 + 31.9 = 113.9 \Omega$$

$$I_T = \frac{V}{R_{eq}} = \frac{15}{113.9} = 0.13 \text{ A}$$

$$I_x = I_T \times \frac{R_3}{R_2 + R_3} = 0.13 \times \frac{47}{100 + 47} = 0.13 \times \frac{47}{147}$$

$$= 0.13 \times 0.31$$

$$I_x = 0.040 \text{ A}$$

Case (ii):- $V_1 = 0, V_2 \neq 0, R_1 = 82 \Omega, R_2 = 100 \Omega, R_3 = 47 \Omega$

$$R_{eq} = R_1 // R_2 + R_3 = \frac{R_1 R_2}{R_1 + R_2} + R_3 = \frac{82 \times 100}{82 + 100} + 47$$

$$= \frac{8200}{182} + 47 = 45.05 + 47 = 92.05 \Omega$$

$$I_T = \frac{V}{R_{eq}} = \frac{10}{92} = 0.108 \text{ A}$$

$$I_y = I_T \times \frac{R_1}{R_1 + R_2} = 0.108 \times \frac{82}{182} = 0.108 \times 0.45 = 0.048 \text{ A}$$

$$I_y = 0.048 \text{ A}$$

Now current through $R_2 = I_x + I_y = 0.040 + 0.048$
 $= 0.088 \text{ A.}$

Precautions:-

- * Check for proper connections before switching ON the supply.
- * Make sure of proper colour of resistor.
- * The terminal of the resistance should be properly connected.

Result:-

Hence Superposition Theorem is verified.

$$A \times 1.0 = \frac{21}{0.811} = \frac{V}{R_{eq}} = I_T$$

$$\frac{F_H}{F_H} \times 1.0 = \frac{F_H \times 1.0}{F_H + 0.01} = \frac{0.9 \times I_T}{0.9 + 0.9} = I_T$$

$$18.0 \times 1.0 =$$

$$A \times 0.0 = 0 \text{ V}$$

$$\frac{F_H}{F_H} \times 0.01 = \frac{F_H \times 0.01}{F_H + 0.01} = \frac{0.9 \times I_T}{0.9 + 0.9} = I_T$$

$$18.0 \times 0.01 = 0.18 \text{ V}$$

$$A \times 0.0 = \frac{0.1}{0.81} = \frac{V}{R_{eq}} = I_T$$

$$F_H \times 0.0 = 0.18 \times 0.01 = \frac{0.18}{0.81} \times 0.01 = 0.0022 \text{ V}$$

$$18.0 \times 0.0 = 0 \text{ V}$$